 


# Introduction: The Problem is Money?



*How to succeed?*


*Try too hard!*

*How to fail?*

*Try too hard!*

*(From American Wisdom)*

Test  
coverage  
function

 

Conclusion:

**“The problem of testing  
can only be contained  
not solved”**

*T. Williams*

# Design for Testability

The problem is - QUALITY:



$$DL = \frac{P_a}{(1-P)^n + P_a} = 1 - (1-P)^{n-m} = 1 - Y^{\frac{n-m}{n}} = 1 - Y^{(1-\frac{m}{n})} = 1 - Y^{(1-T)}$$

$n$  - number of defects

$m$  - number of faults tested

$P$  - probability of a defect

$P_a$  - probability of accepting a bad product

$T$  - test coverage

$$P_a = (1-P)^m - (1-P)^n$$

$$Y = (1-P)^n$$

# Testability of Design Types

---

## General important relationships:

- **T (Sequential logic) < T (Combinational logic)**  
*Solutions:* Scan-Path design strategy
- **T (Control logic) < T (Data path)**  
*Solutions:* Data-Flow design, Scan-Path design strategies
- **T (Random logic) < T (Structured logic)**  
*Solutions:* Bus-oriented design, Core-oriented design
- **T (Asynchronous design) < T (Synchronous design)**

# Testability Estimation Rules of Thumb

---

## Circuits less controllable


- Decoders
- Circuits with feedback
- Counters
- Clock generators
- Oscillators
- Self-timing circuits
- Self-resetting circuits

## Circuits less observable

- Circuits with feedback
- Embedded
  - RAMs
  - ROMs
  - PLAs
- Error-checking circuits
- Circuits with redundant nodes


# Fault Redundancy

## Hazard control circuit:

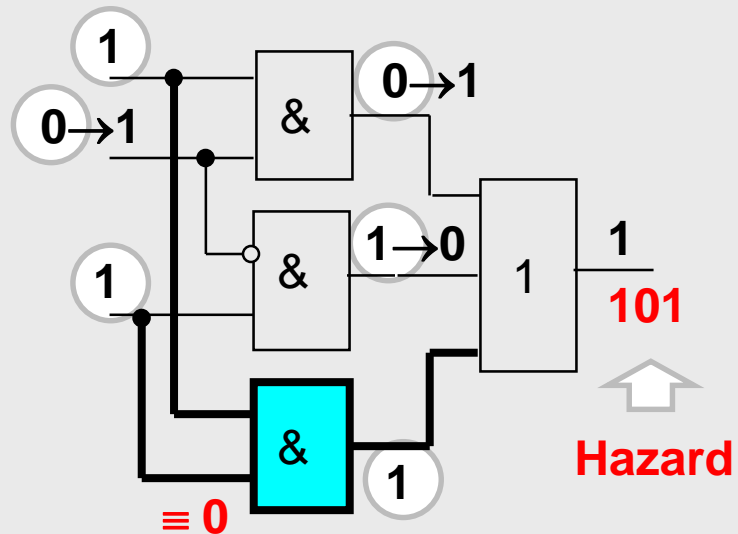

Redundant AND-gate  
**Fault  $\equiv 0$  is not testable**

## Error control circuitry:

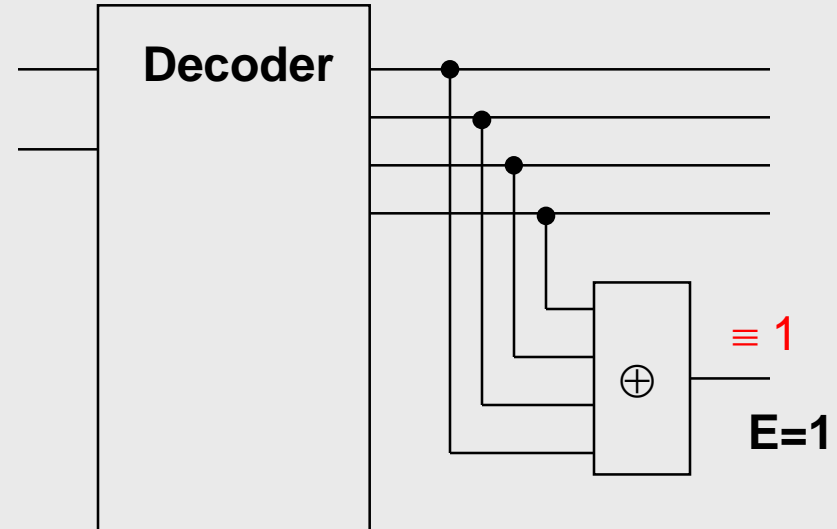

**E = 1 if decoder is fault-free**  
**Fault  $\equiv 1$  is not testable**

# Hard to Test Faults

## Evaluation of testability:


- **Controllability**

- $C_0(i)$
- $C_1(j)$

- **Observability**

- $O_Y(k)$
- $O_Z(k)$

- **Testability**

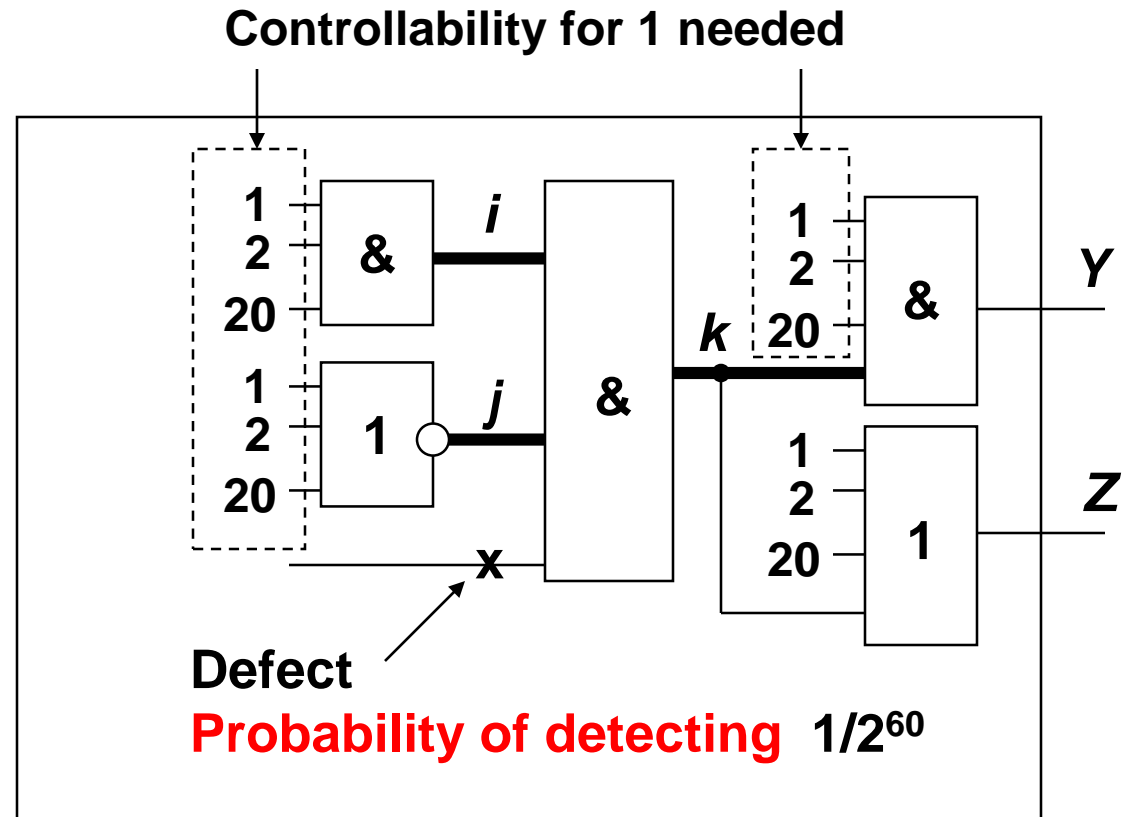






# Probabilistic Testability Measures

## Controllability calculation:

Value: minimum number of nodes that must be set in order to produce 0 or 1


For inputs:  $C_0(i) = p(x_i=0)$   $C_1(i) = p(x_i=1) = 1 - p(x_i=0)$

     For other signals: recursive calculation rules:



# Calculation of Signal Probabilities

Straightforward methods:

 

For all inputs:  $p_k = 1/2$

Calculation gate by gate:

$$p_a = 1 - p_1 p_2 = 0,75,$$

$$p_b = 0,75, p_c = 0,4375, p_y = 0,22$$

Parker - McCluskey algorithm:

$$p_y = p_c p_2 = (1 - p_a p_b) p_2 =$$
$$= (1 - (1 - p_1 p_2) (1 - p_2 p_3)) p_2 =$$


$$= p_1 p_2^2 + p_2^2 p_3 - p_1 p_2^3 p_3 =$$

$$= p_1 p_2 + p_2 p_3 - p_1 p_2 p_3 = 0,38$$



# Probabilistic Testability Measures

Parker-McCluskey:

 

For all inputs:  $p_k = 1/2$

**Observability:**

$$\begin{aligned}
 p(\partial y / \partial a = 1) &= p_b p_2 = \\
 &= (1 - p_2 p_3) p_2 = p_2 - p_2^2 p_3 \\
 &= p_2 - p_2 p_3 = 0,25
 \end{aligned}$$

**Testability:**

$$\begin{aligned}
 p(a \equiv 1) &= p(\partial y / \partial a = 1) (1 - p_a) = \\
 &= (p_2 - p_2 p_3)(p_1 p_2) = \\
 &= p_1 p_2^2 - p_1 p_2^2 p_3 = \\
 &= p_1 p_2 - p_1 p_2 p_3 = 0,125
 \end{aligned}$$

# Calculation of Signal Probabilities


## Cutting method

Idea:

- Complexity of exact calculation is reduced by using lower and higher bounds of probabilities

Technique:

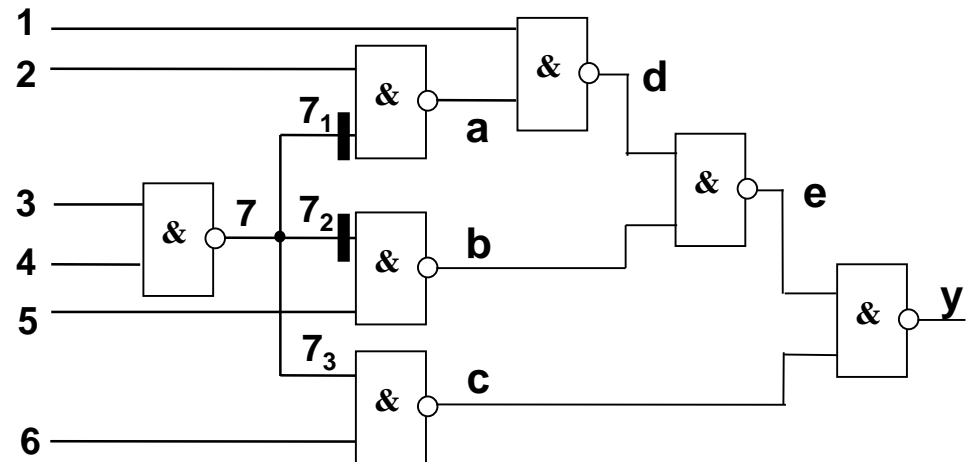- Reconvergent fan-outs are cut **except of one**
- Probability range of  $[0,1]$  is assigned to all the cut lines
- The bounds are propagated by straightforward calculation




*Lower and higher bounds for the probabilities of the cut lines:*

$$p_{7_1} := (0;1), \quad p_{7_2} := (0;1), \quad p_{7_3} := 0,75$$
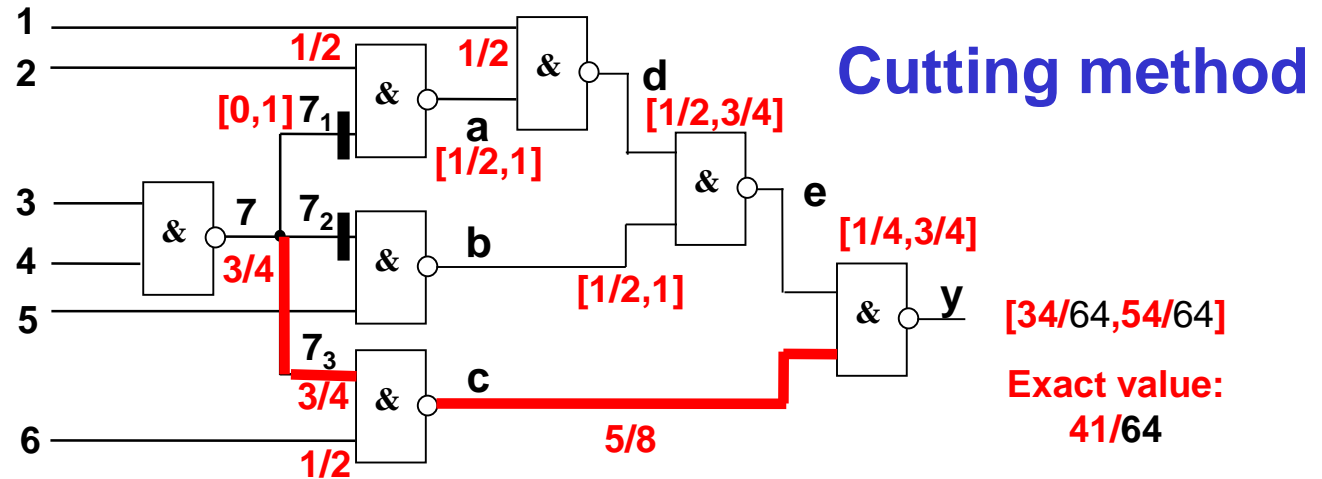
# Calculation of Signal Probabilities

- For all inputs:  $p_k = 0,5$
- Reconvergent fan-outs are cut except of one –  $7_1$  and  $7_2$
- Probability range of  $[0,1]$  is assigned to all the cut lines -  $7_1$  and  $7_2$
- The bounds are propagated by straightforward calculation




## Calculation steps:

$p_k$	$[p_{LB}, p_{HB})$	Exact $p_k$	$p_k$	$[p_{LB}, p_{HB})$	Exact $p_k$
$p_7$	$3/4$	$3/4$	$p_b$	$[1/2, 1]$	$5/8$
$p_{71}$	$[0, 1]$	$3/4$	$p_c$	$5/8$	$5/8$
$p_{72}$	$[0, 1]$	$3/4$	$p_d$	$[1/2, 3/4]$	$11/16$
$p_{73}$	$3/4$	$3/4$	$p_e$	$[1/4, 3/4]$	$19/32$
$p_a$	$[1/2, 1]$	$5/8$	$p_y$	$[34/64, 54/64]$	$41/64$

# Calculation of Signal Probabilities

## Method of conditional probabilities

 

$$P(y) = p(y/x=0) p(x=0) + p(y/x=1) p(x=1)$$

### *Idea of the method:*

**Two conditional probabilities** are calculated along the paths (NB! not bounds as in the case of the cutting method)

Since no reconvergent fanouts are on the paths, no danger for signal correlations

Probability for  $-y$

Conditions –  $x \in$  set of conditions


$$p(y) = \sum_{i \in (0,1)} p(y/(x=i)) p(x=i)$$

Conditional probability

# Calculation of Signal Probabilities
 
## Method of conditional probabilities

$$p(y) = \sum_{i \in \{0,1\}} p(y/(x=i)) p(x=i)$$




**NB! Probabilities**

$P_k = [P_k^* = p(x_k/x_7=0), P_k^{**} = p(x_k/x_7=1)]$

are propagated, not bounds as in the cutting method.

For all inputs:  $p_k = 1/2$

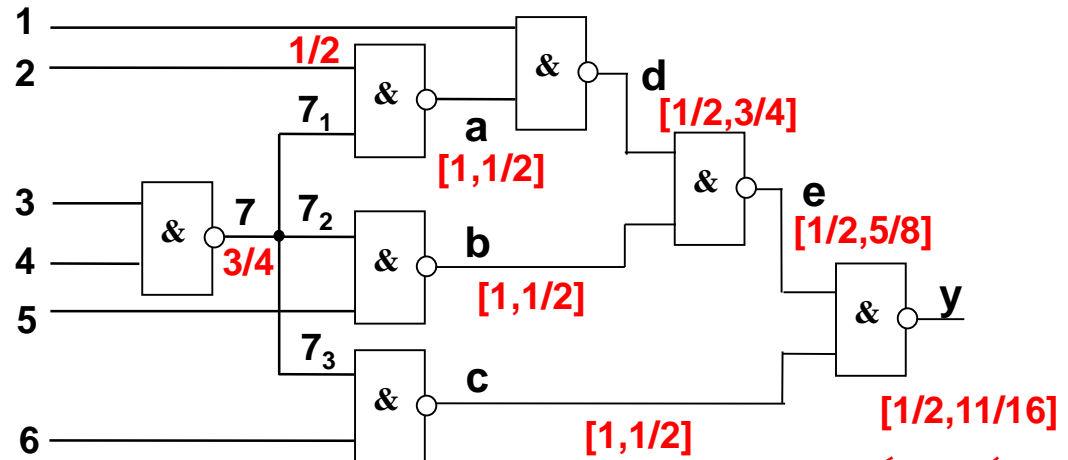


$P_k$	$[P_k^*, P_k^{**}]$	$P_k$	$[P_k^*, P_k^{**}]$
$P_7$		$P_b$	$[1, 1/2]$
$P_{71}$		$P_c$	$[1, 1/2]$
$P_{72}$		$P_d$	$[1/2, 3/4]$
$P_{73}$		$P_e$	$[1/2, 5/8]$
$P_a$	$[1, 1/2]$	$P_y$	$[1/2, 11/16]$

$$p_y = p(y/x_7=0)(1 - p_7) + p(y/x_7=1)p_7 = (1/2 \times 1/4) + (11/16 \times 3/4) = 41/64$$


# Ad Hoc Design for Testability Techniques

## Method of Test Points:

 


Block 1 is not observable,  
Block 2 is not controllable
 
## Improving controllability and observability:


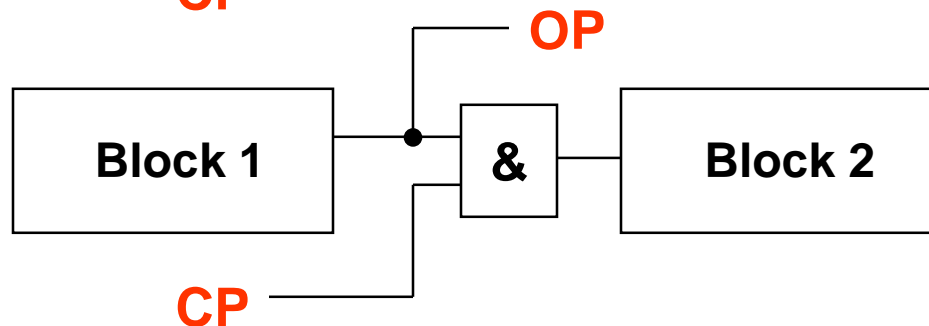
### 1- controllability:

CP = 0 - normal working mode  
CP = 1 - controlling Block 2  
with signal 1



### 0- controllability:

CP = 1 - normal working mode  
CP = 0 - controlling Block 2  
with signal 0

# Ad Hoc Design for Testability Techniques


## Multiplexing monitor points:

To reduce the number of output pins for observing monitor points, multiplexer can be used:

$2^n$  observation points are replaced by a **single output** and **n inputs** to address a selected observation point
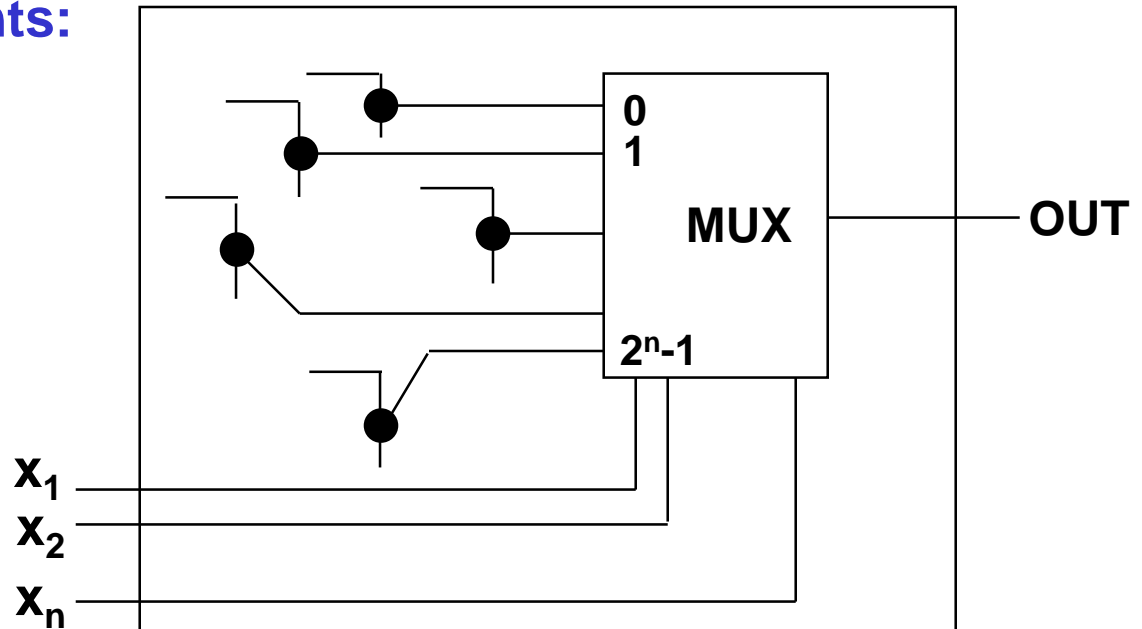
## Disadvantage:

Only one observation point can be observed at a time



Number of additional pins:  $(n + 1)$

Number of observable points:  $[2^n]$

**Advantage:**  $(n + 1) \ll 2^n$

# Ad Hoc Design for Testability Techniques


## Multiplexing monitor points:

To reduce the number of output pins for observing monitor points, multiplexer can be used:

To reduce the number of inputs, a **counter** (or a shift register) can be used to drive the address lines of the multiplexer
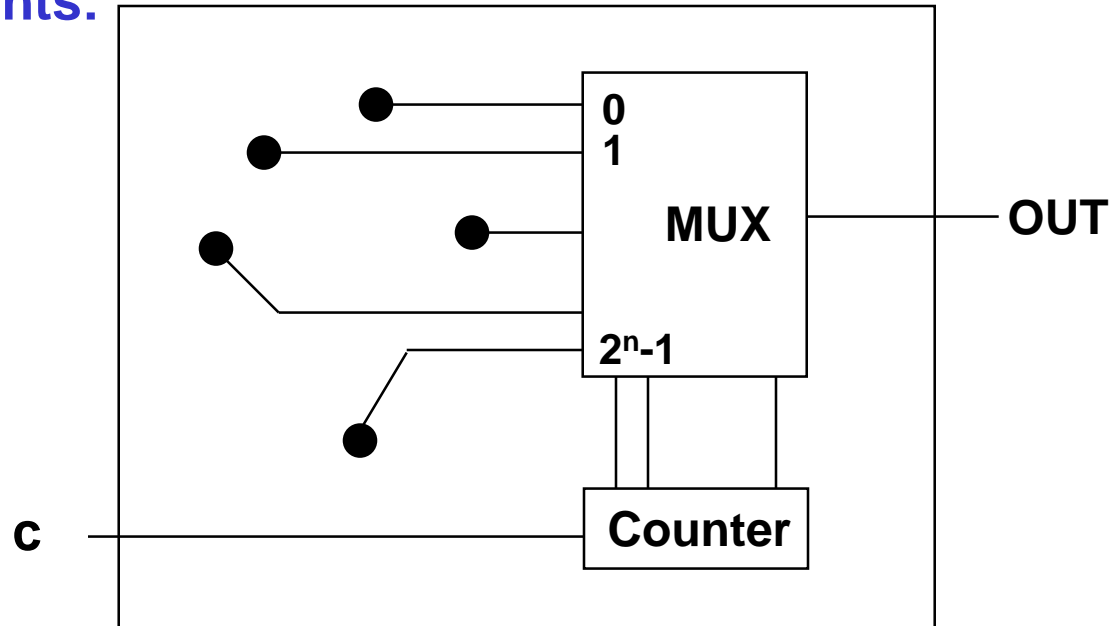
### Disadvantage:

Only one observation point can be observed at a time




Number of additional pins: **2**  
Number of observable points: **[ $2^n$ ]**

**Advantage:**  $2 \ll 2^n$



# Ad Hoc Design for Testability Techniques
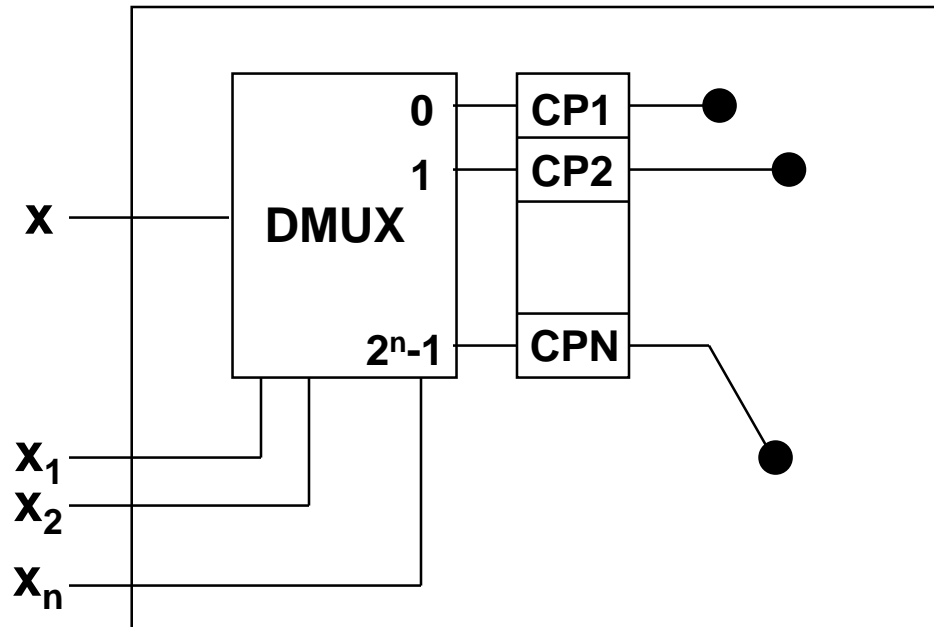
## Demultiplexer for implementing control points:



To reduce the number of input pins for controlling testpoints, **demultiplexer** and a **latch register** can be used.

### Disadvantage:


N clock times are required between test vectors to set up the proper control values

Number of additional pins:  $(n + 1)$   
Number of control points:  $2^{n-1} < N \leq 2^n$

**Advantage:**  $(n + 1) \ll N$

# Ad Hoc Design for Testability Techniques
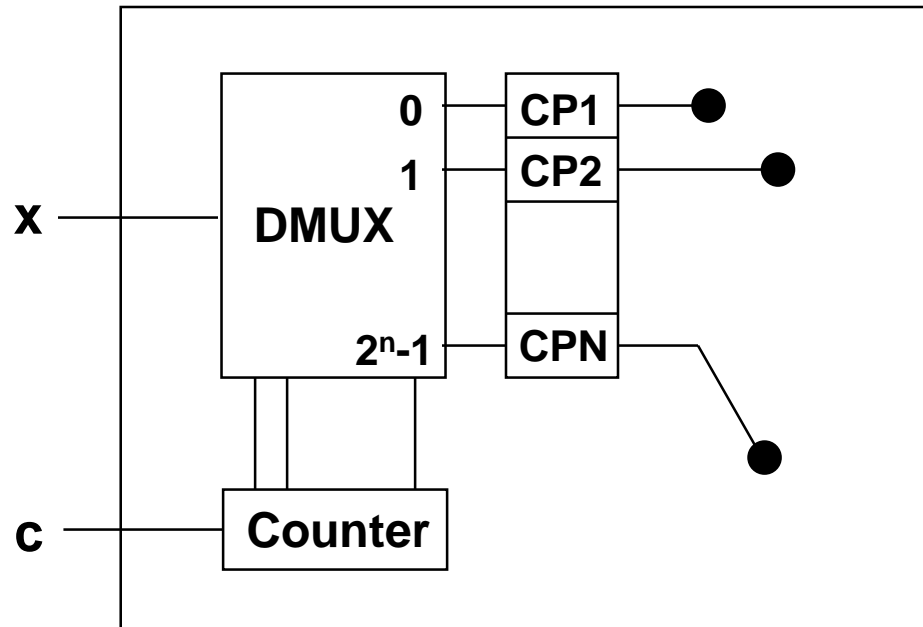
## Demultiplexer for implementing control points:



Number of additional pins: **2**  
Number of control points: **N**

**Advantage:**  $2 \ll N$

To reduce the number of input pins for controlling testpoints, **demultiplexer** and a **latch register** can be used.

To reduce the number of inputs for addressing, a **counter** (or a **shift register**) can be used to drive the address lines of the demultiplexer


### Disadvantage:

$N$  clock times are required between test vectors to set up the proper control values
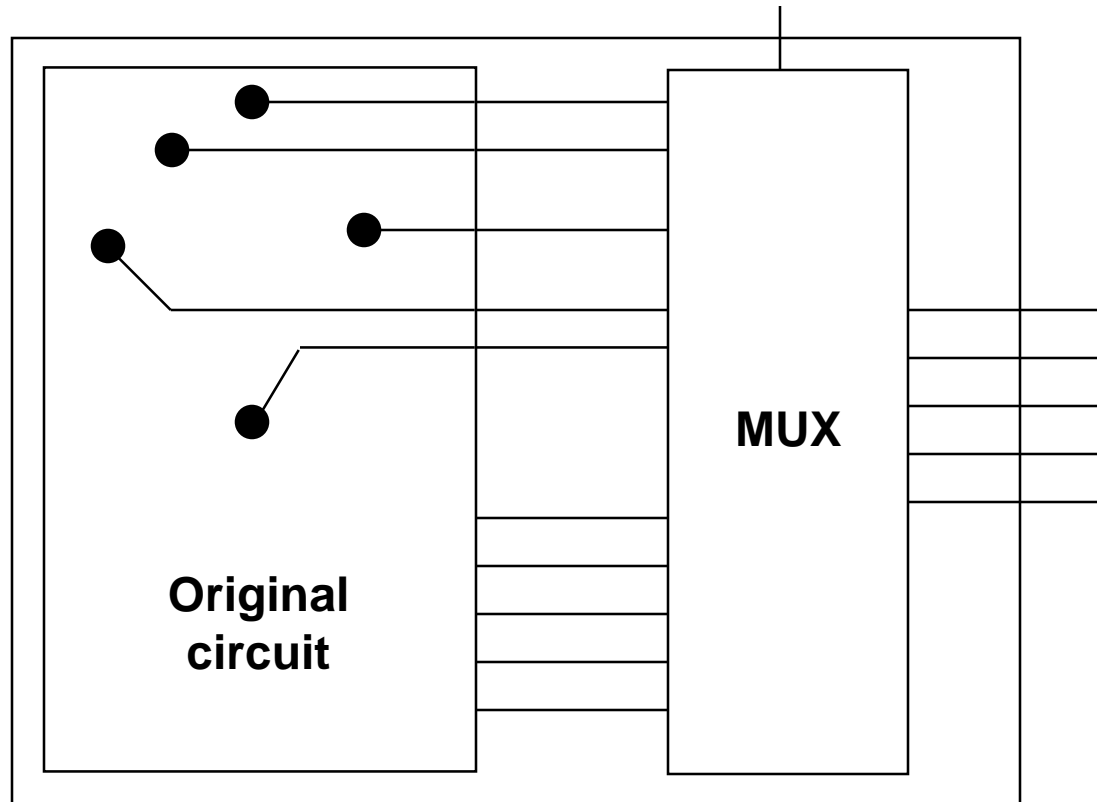
# Time-sharing of outputs for monitoring

To reduce the number of output pins for observing monitor points, time-sharing of working outputs can be introduced: no additional outputs are needed


To reduce the number of inputs, again **counter** or shift **register** can be used if needed



Number of additional pins: **1**  
Number of control points: **N**

**Advantage:**  $1 \ll N$

# Time-sharing of inputs for controlling

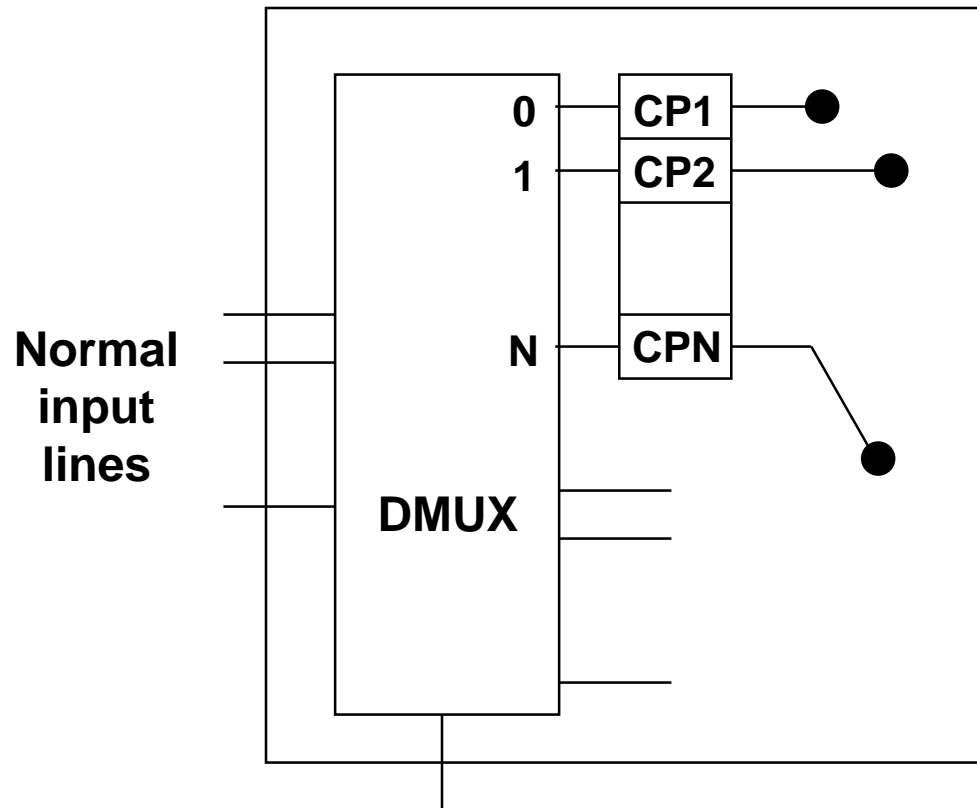

To reduce the number of input pins for controlling test points, time-sharing of working inputs can be introduced.

To reduce the number of inputs for driving the address lines of **demultiplexer, counter** or **shift register** can be used if needed

Number of additional pins: **1**  
Number of control points: **N**

**Advantage:**  $1 \ll N$


# Example: DFT with MUX-s and DMUX-s

---
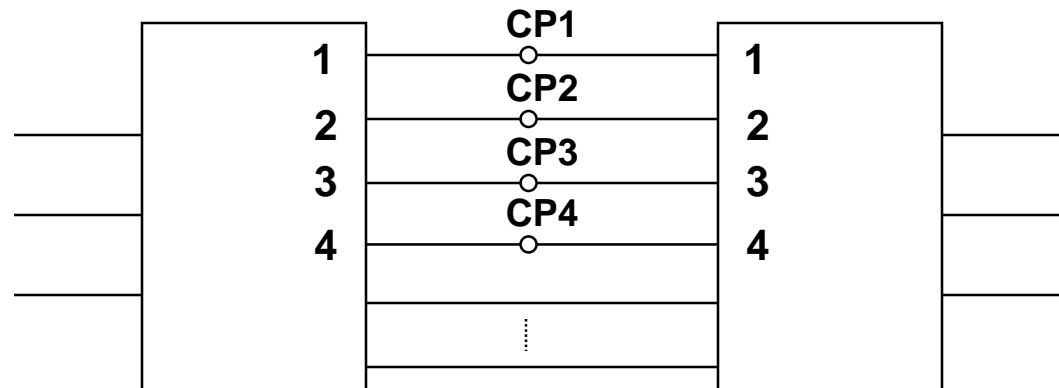
## Given a circuit:

- CP1 and CP2 are not controllable
- CP3 and CP4 are not observable

**DFT task:** Improve the testability by using a **single control input**, no additional inputs/outputs allowed



# Example: DFT with MUX-s and DMUX-s


Given a circuit:

CP3 and CP4 are **not observable**

→ Improving the observability

Coding:

T	Mode	MUX
0	Norm.	0
1	Test	1

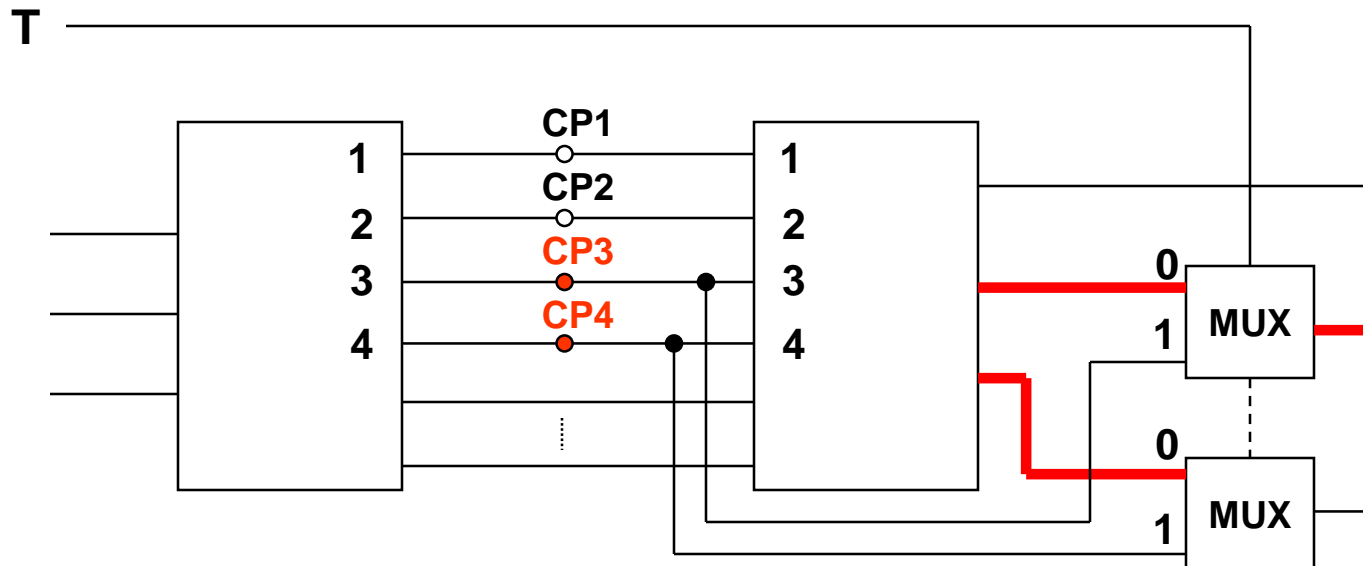


**Result:** A single pin **T** is needed

# Example: DFT with MUX-s and DMUX-s

Given a circuit: CP1 and CP2 are **not controllable** → Improving the controllability


Coding:

Q	Mode	DMUX	MUX
00	Norm.	1	1
01	Contr	0	x
10	Test	1	0

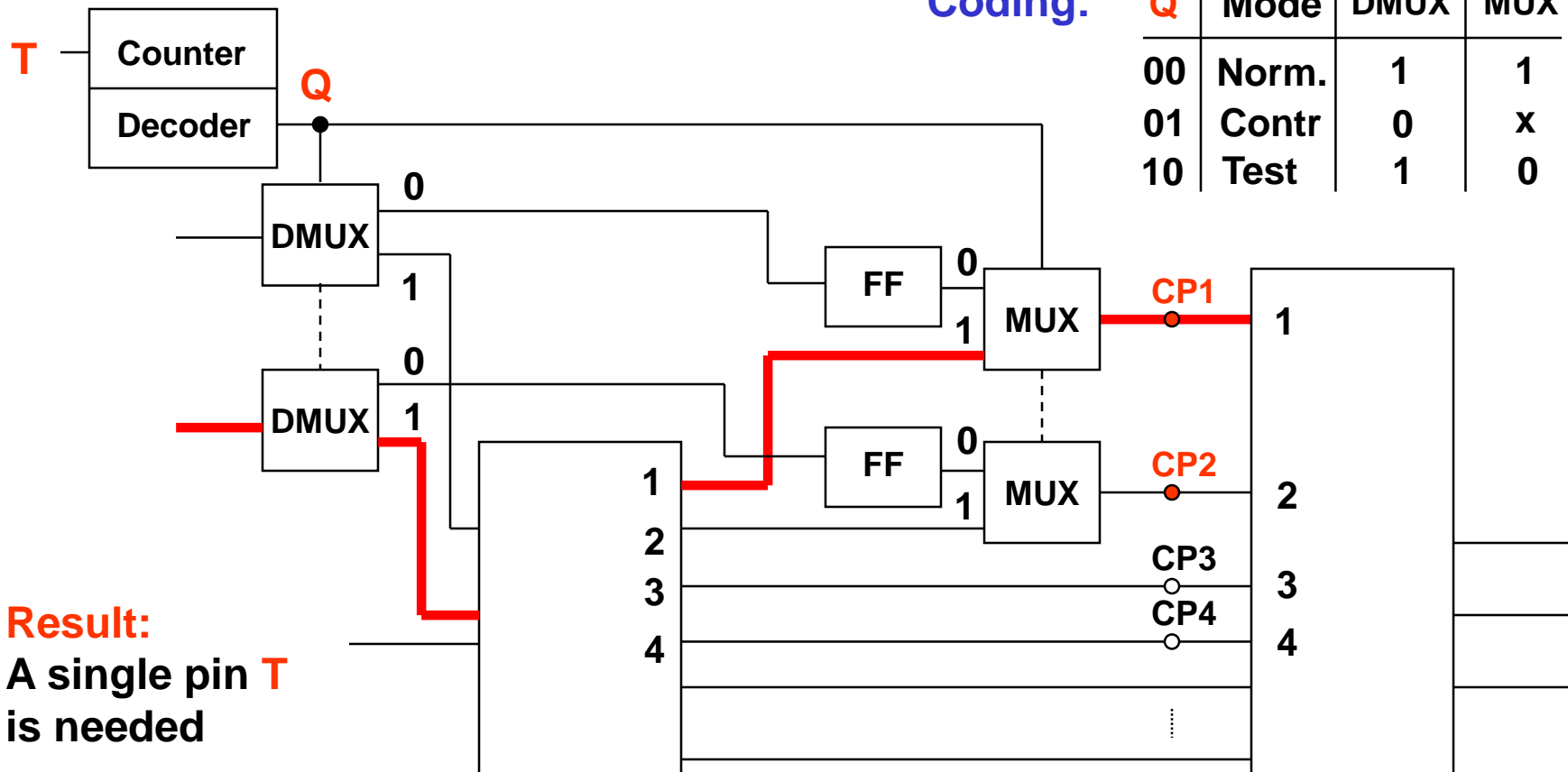

**Result:**  
A single pin **T**  
is needed

# Example: DFT with MUX-s and DMUX-s

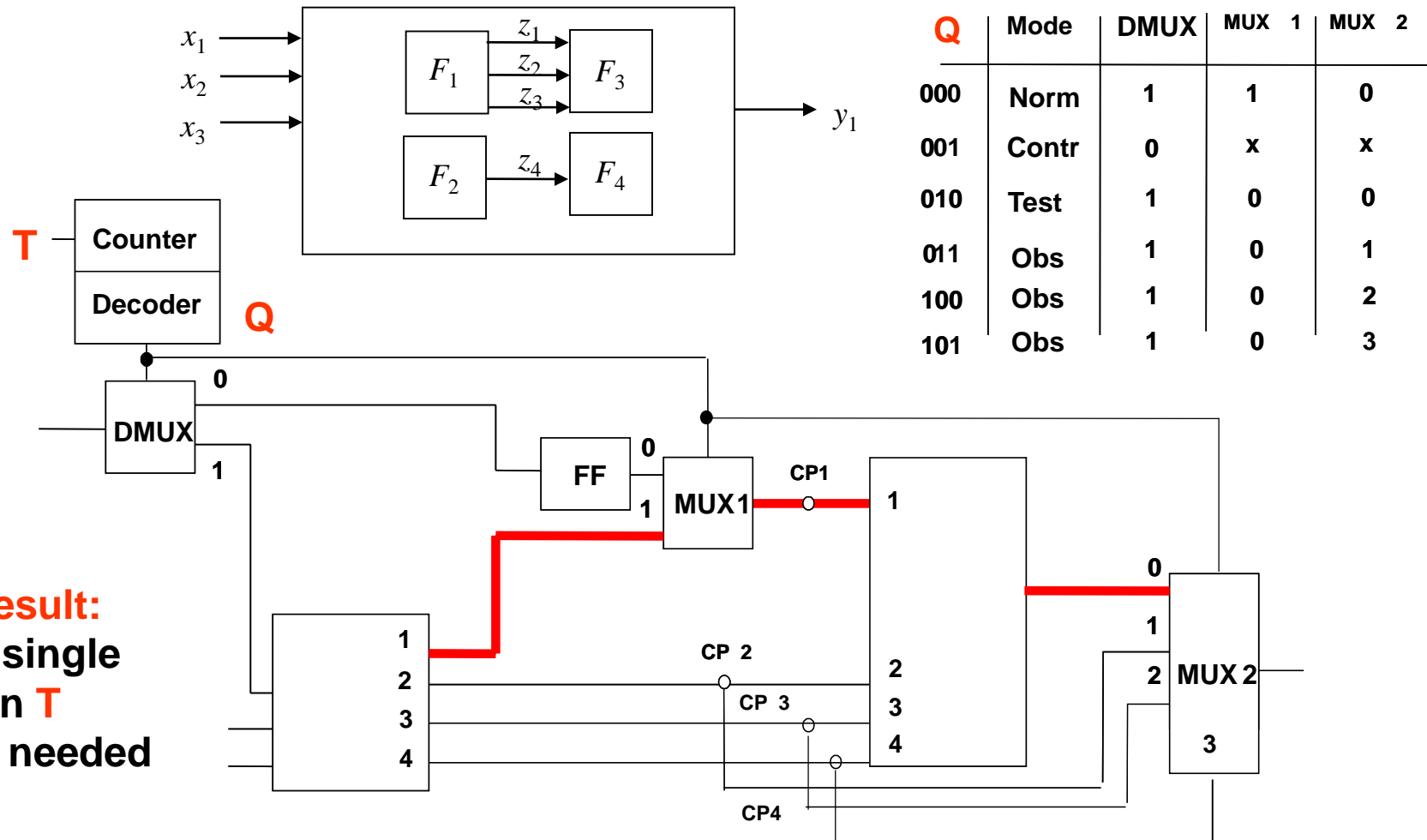



# Ad Hoc Design for Testability Techniques

## Logical redundancy:


### Redundancy should be avoided:

- If a redundant fault occurs, it may invalidate some test for nonredundant faults
- Redundant faults cause difficulty in calculating fault coverage
- Much test generation time can be spent in trying to generate a test for a redundant fault

### Redundancy intentionally added:

- To eliminate hazards in combinational circuits
- To achieve high reliability (using error detecting circuits)

### Hazard control circuitry:

 


Redundant AND-gate  
Fault  $\equiv 0$  not testable

**Additional control input added:**  
**T = 1** - normal working mode  
**T = 0** - testing mode

# Ad Hoc Design for Testability Techniques


## Fault redundancy:

### Error control circuitry:

 


$E = 1$  if decoder is fault-free  
Fault  $\equiv 1$  **not testable**

### Testable error control circuitry:

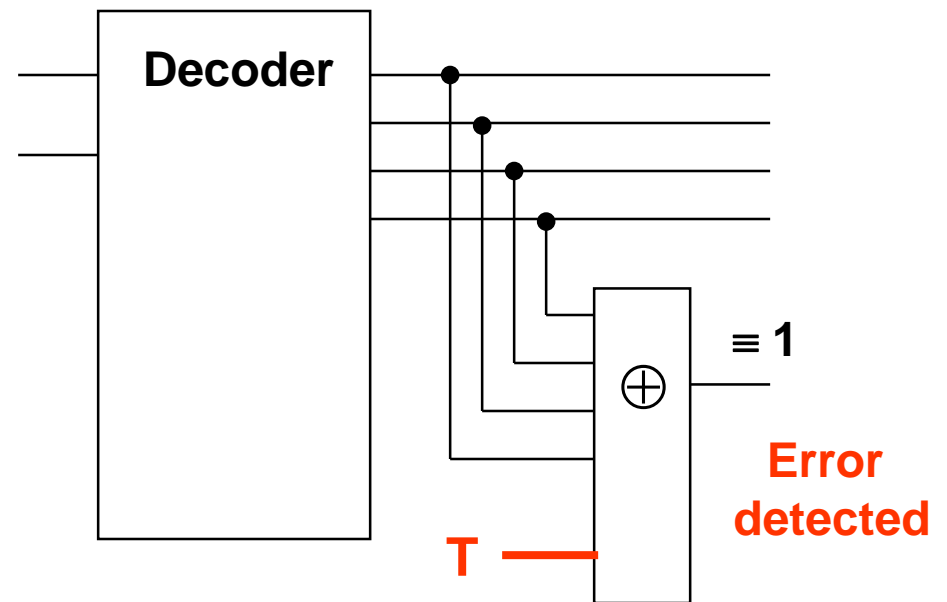

**Additional control input added:**  
 $T \equiv 0$  - normal working mode  
 $T = 1$  - testing mode

# Scan-Path Design

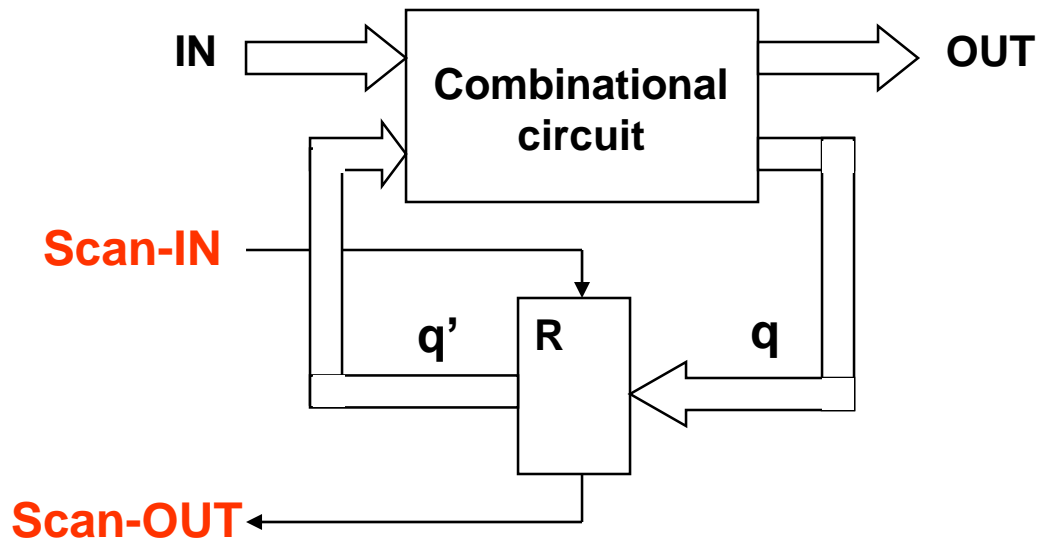

The complexity of testing is a function of the number of feedback loops and their length

The longer a feedback loop, the more clock cycles are needed to initialize and sensitize patterns


**Scan-register** is a register with both shift and parallel-load capability

T = 0 - normal working mode

T = 1 - scan mode



**Normal mode** : flip-flops are connected to the combinational circuit

 **Test mode**: flip-flops are disconnected from the combinational circuit and connected to each other to form a shift register



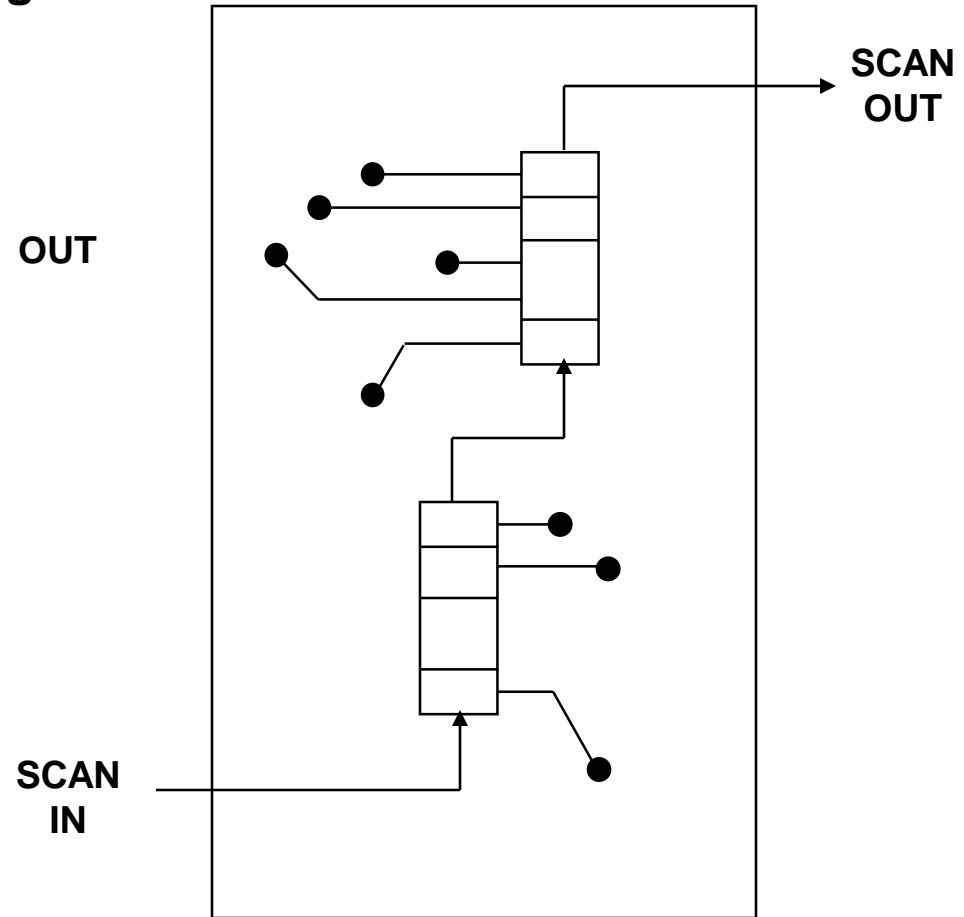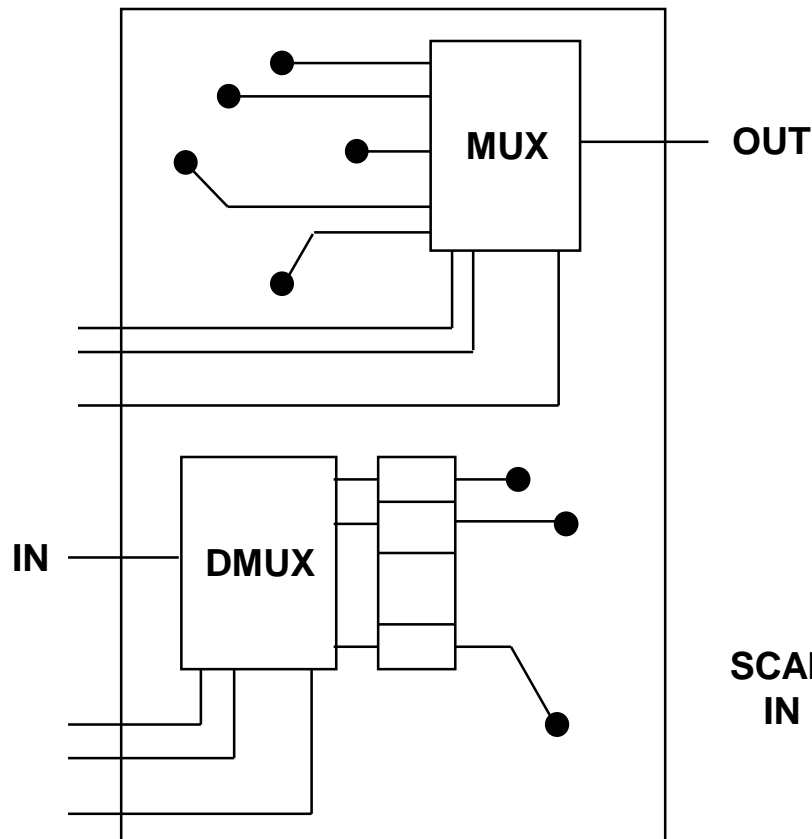
# Scan-Path Design and Testability

Two possibilities for improving controllability/observability



# Parallel Scan-Path

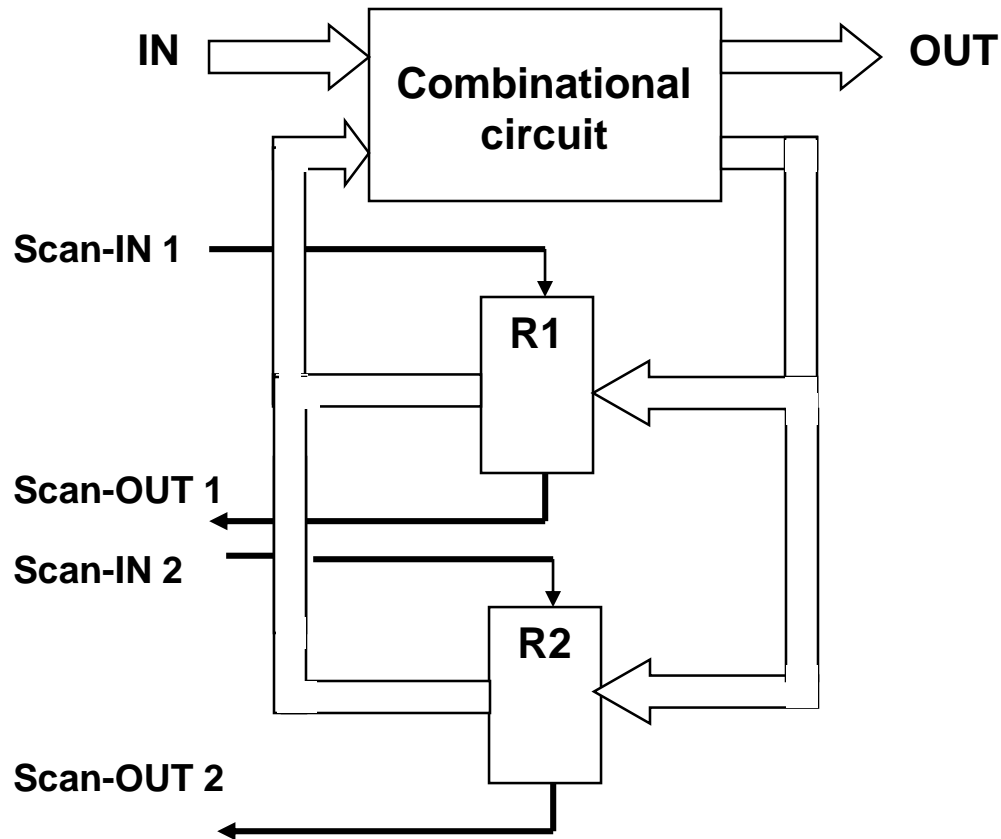


In **parallel scan path** flip-flops can be organized in more than one scan chain

**Advantage:** time ↓

**Disadvantage:** # pins ↑

# Partial Scan-Path

 


In **partial scan** instead of full-scan, it may be advantageous to scan **only some** of the flip-flops

*Example:* **counter**  
– even bits joined in the scan-register

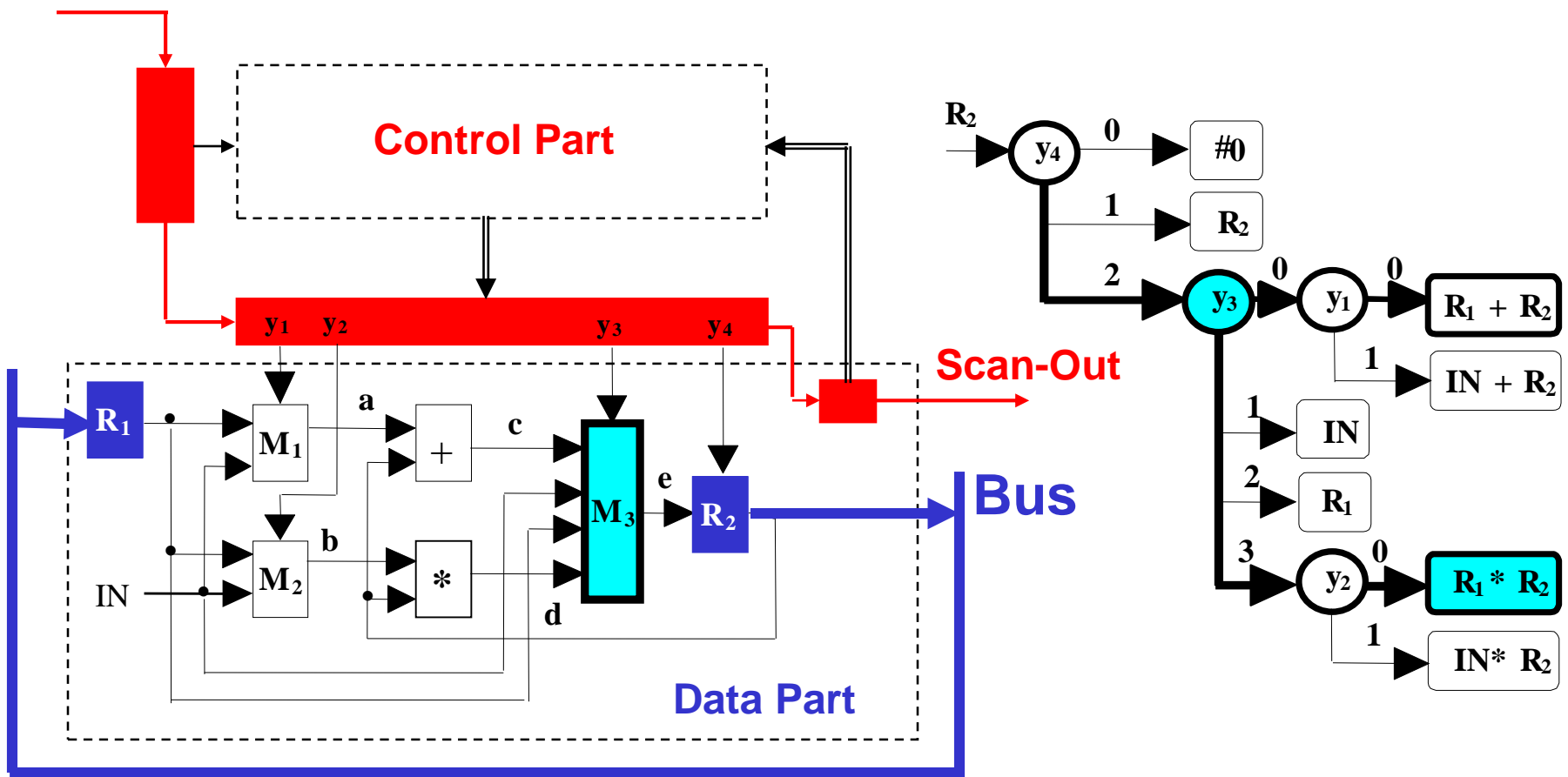
# Partial Scan Path

**Scan-In** Hierarchical test generation with Scan-Path:




# Testing with Minimal DFT
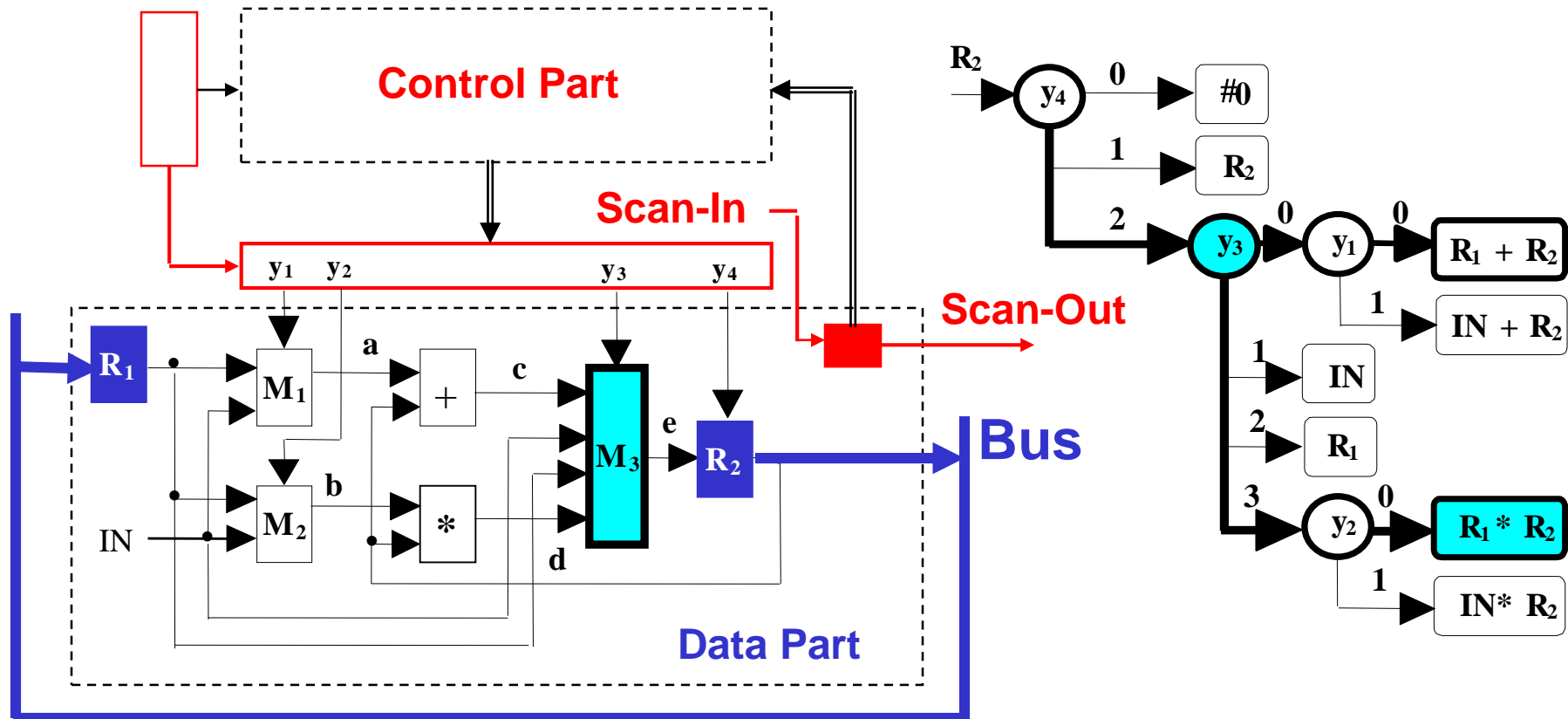
## Hierarchical test generation with Scan-Path:





# Random Access Scan

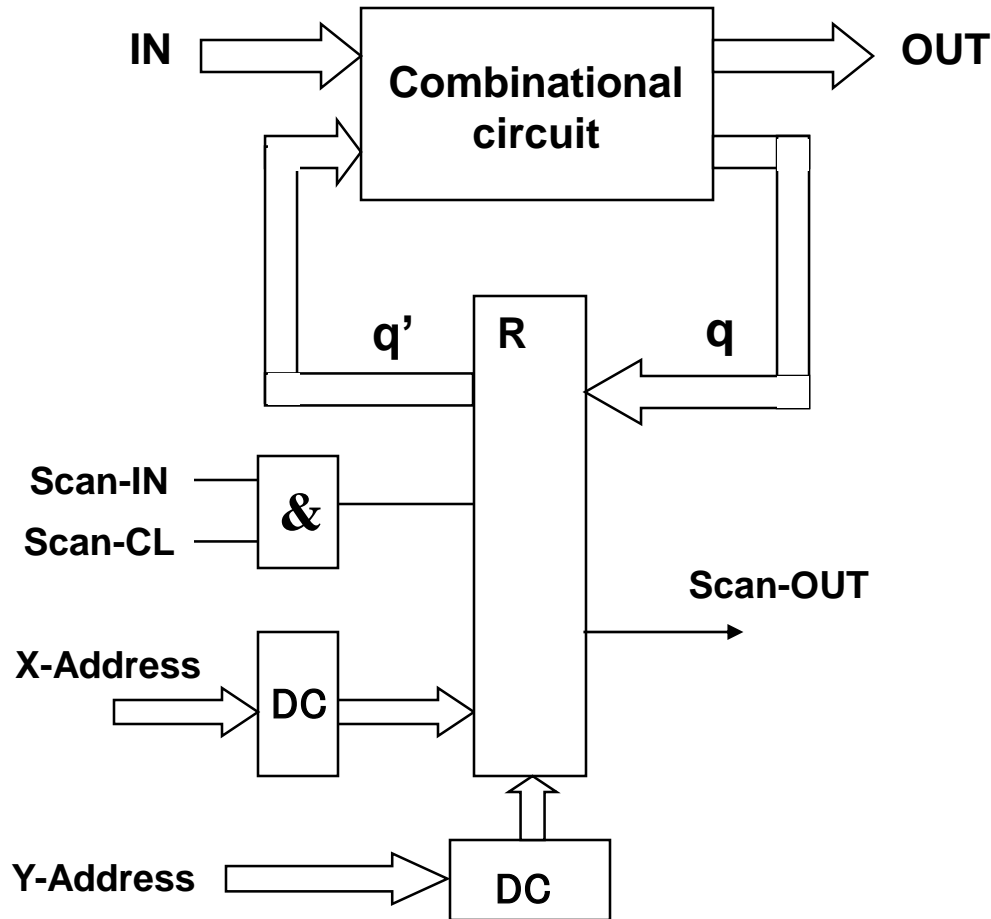



In random access scan each flip-flop in a logic network is selected individually by an address for control and observation of its state

Example:

Delay fault testing
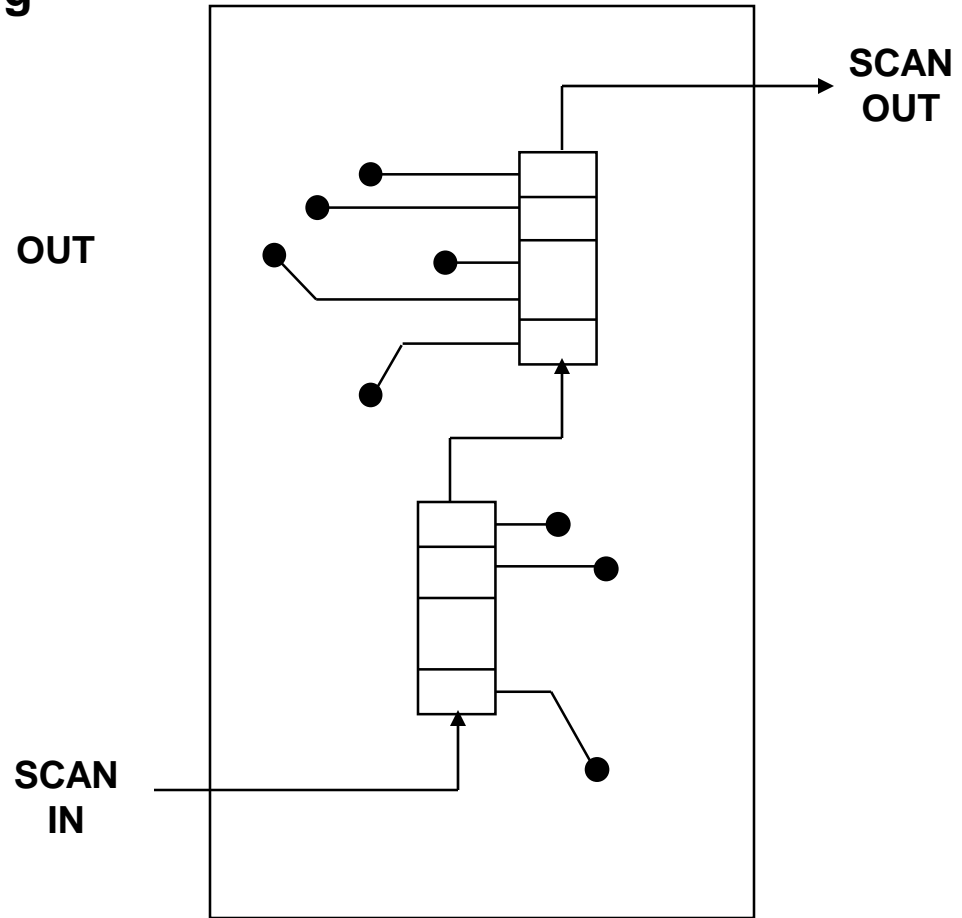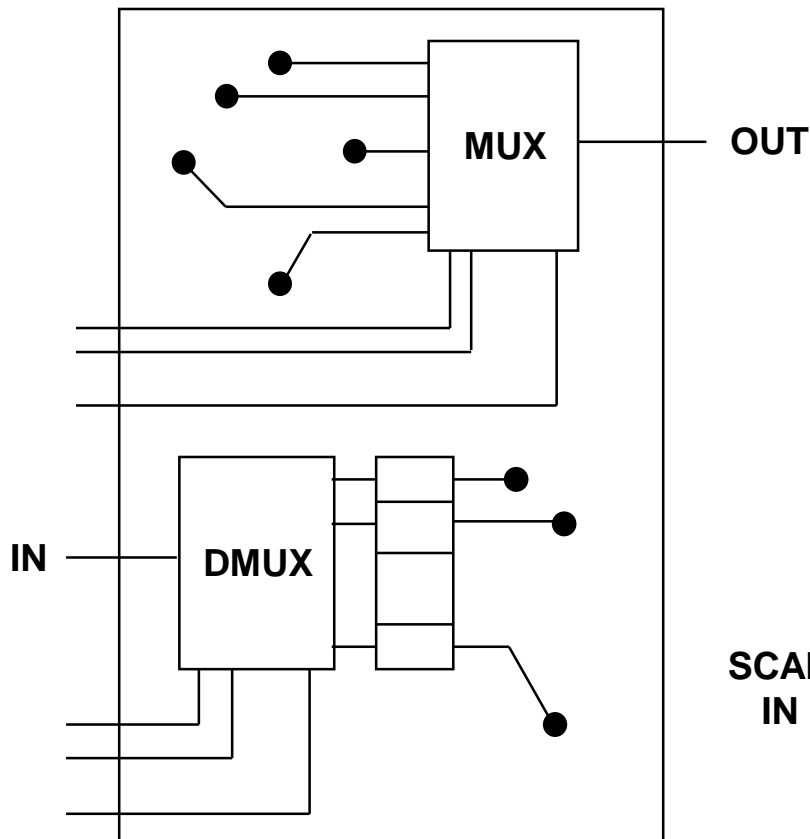
# Improving Testability by Inserting CPs

**Two possibilities** for improving controllability/observability



# Built-In Self-Test

---


- **Motivations for BIST:**

- **Need for a cost-efficient testing** (general motivation)
- Doubts about the stuck-at fault model
- Increasing difficulties with TPG (Test Pattern Generation)
- Growing volume of test pattern data
- Cost of ATE (Automatic Test Equipment)
- Test application time
- **Gap between** tester and UUT (Unit Under Test) **speeds**

- **Drawbacks of BIST:**


- **Additional pins** and silicon area needed
- Decreased reliability due to increased silicon area
- **Performance impact** due to additional circuitry
- Additional design time and cost

# SoC BIST

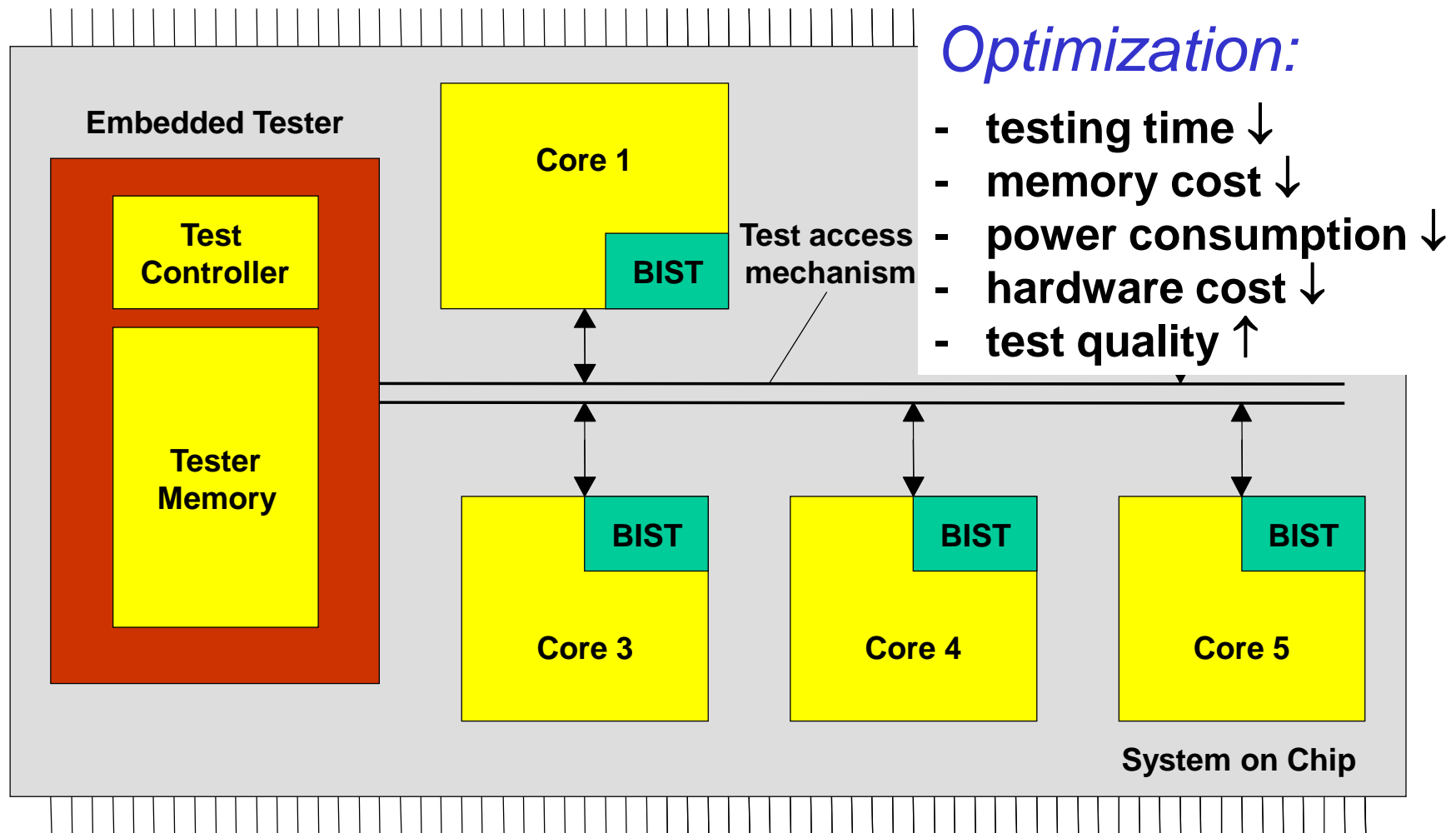


# General Architecture of BIST

---

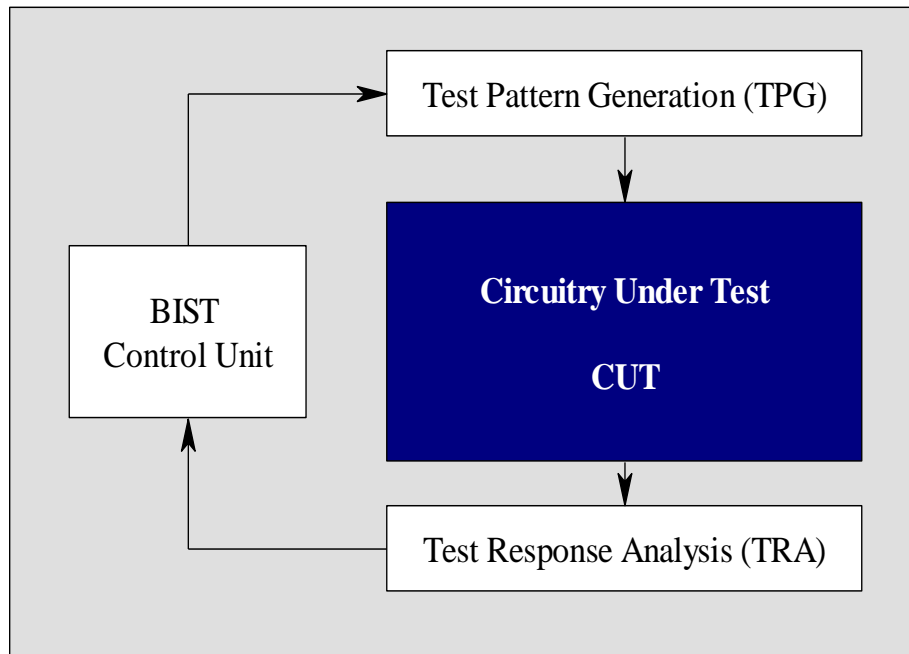

- **BIST components:**
  - Test pattern generator (TPG)
  - Test response analyzer (TRA)
- **TPG & TRA are usually implemented as linear feedback shift registers (LFSR)**
- **Two widespread schemes:**
  - test-per-scan
  - test-per-clock

# Built-In Self-Test

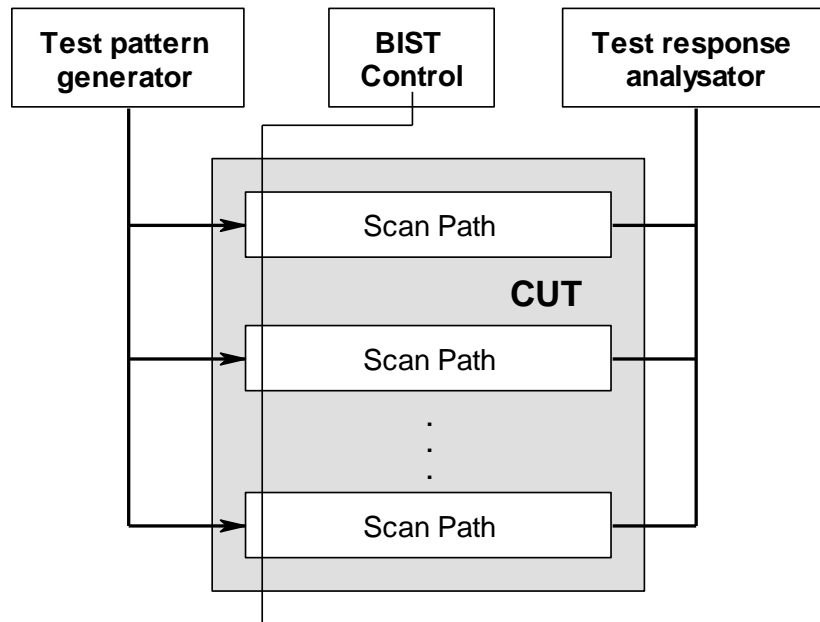

## Test per Scan:

### Initial test set:

T1: 1100

T2: 1010

T3: 0101

T4: 1001

### Test application:


1100 T 1010 T 0101T 1001 T

Number of clocks =  $(4 \times 4) + 4 = 20$

- Assumes existing scan architecture
- Drawback:
  - Long test application time

# Built-In Self-Test


## Test per Clock:

 

- **Initial test set:**

- T1: 1100
- T2: 1010
- T3: 0101
- T4: 1001


- **Test application:**

 

- **Number of clocks = 8 < 20**

# Pattern Generation

## Pseudorandom test generation by LFSR:

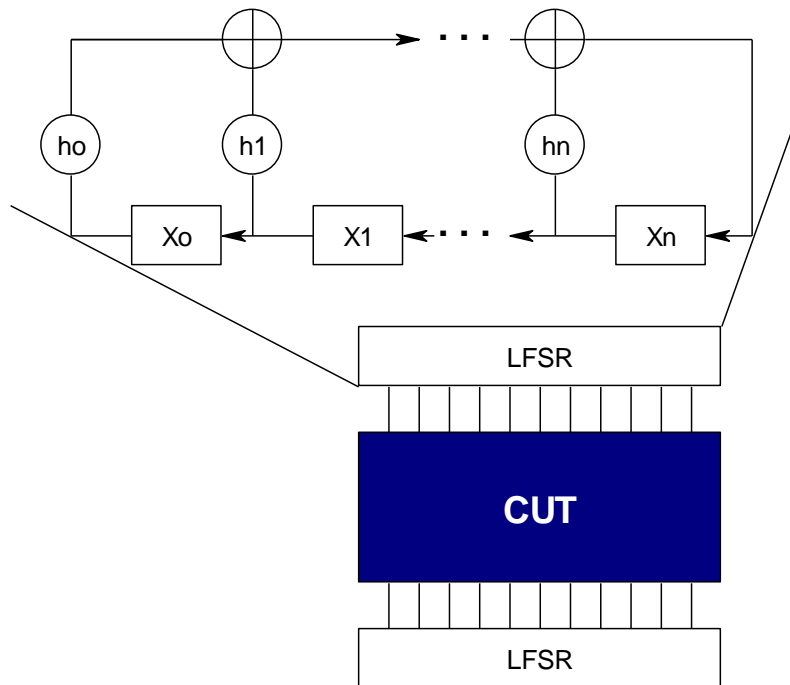


- **Using special LFSR registers**
  - Test pattern generator
  - Signature analyzer
- **Several proposals:**
  - BILBO
  - CSTP
- **Main characteristics of LFSR:**
  - polynomial
  - initial state
  - test length




# Pseudorandom Test Generation

## LFSR – Linear Feedback Shift Register:

Standard LFSR

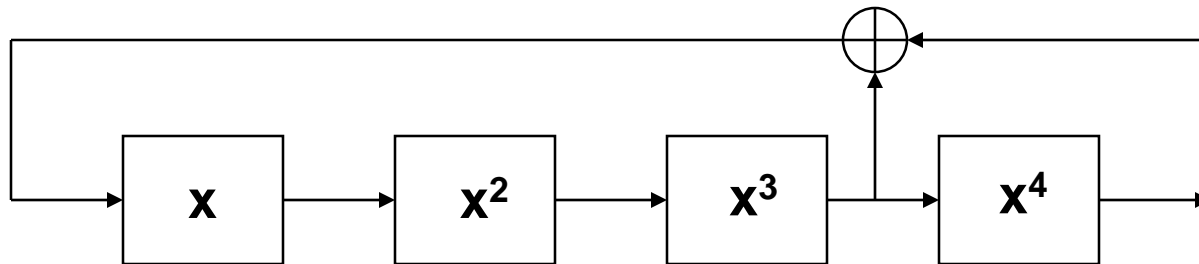

Modular LFSR

 


**Polynomial:  $P(x) = x^4 + x^3 + 1$**

# Pseudorandom Test Generation

## LFSR – Linear Feedback Shift Register:

Why modular LFSR is useful for BIST?

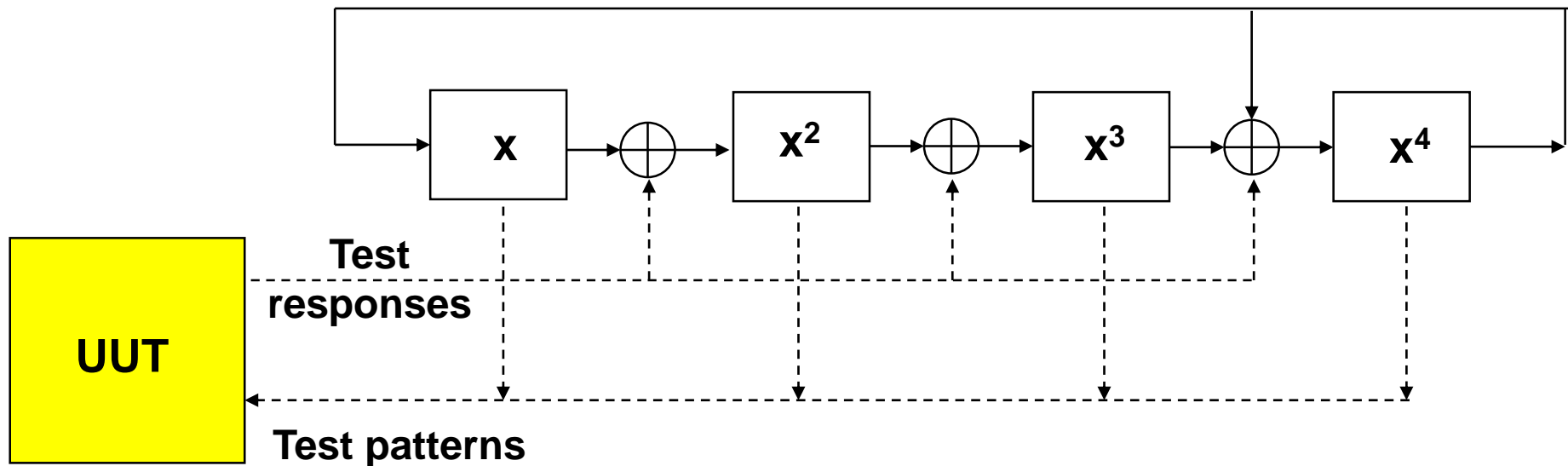

**Polynomial:**  $P(x) = x^4 + x^3 + 1$

# BILBO BIST Architecture


## Working modes:

**B1 B2**


<b>0</b>	<b>0</b>	<b>Normal mode</b>
<b>0</b>	<b>1</b>	<b>Reset</b>
<b>1</b>	<b>0</b>	<b>Test mode</b>
<b>1</b>	<b>1</b>	<b>Scan mode</b>

## Testing modes:


<b>CC1:</b>	<b>LFSR 1 - TPG</b>
	<b>LFSR 2 - SA</b>
<b>CC2:</b>	<b>LFSR 2 - TPG</b>
	<b>LFSR 1 - SA</b>

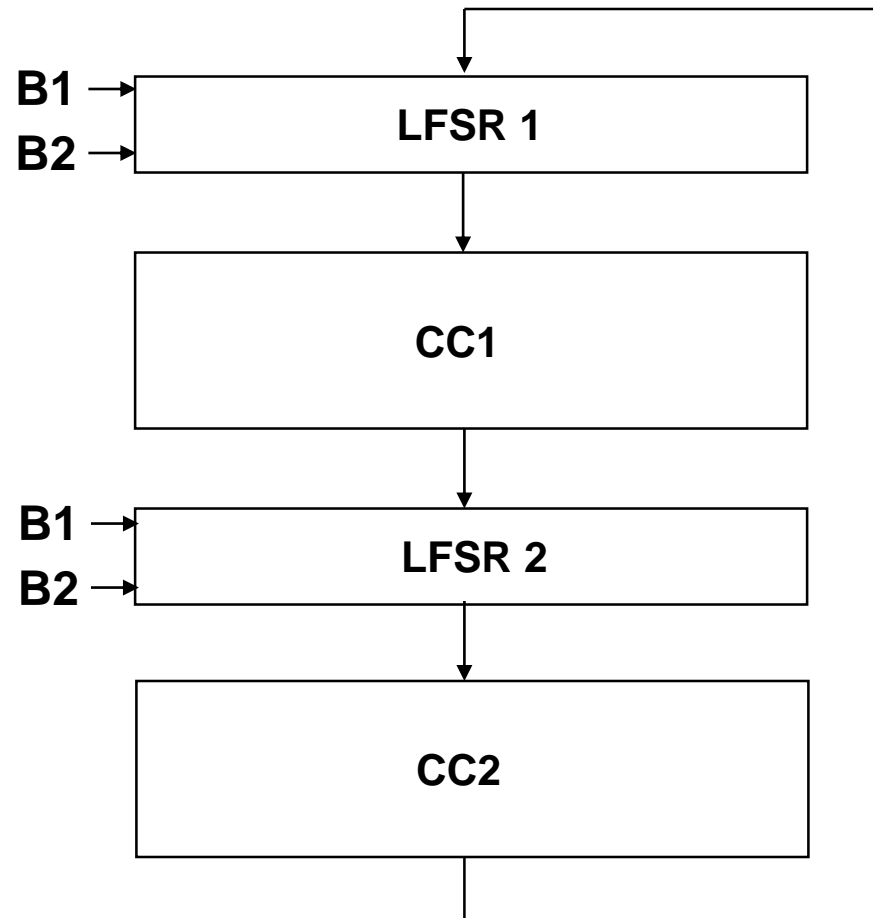

# Reconfiguration of the LFSR

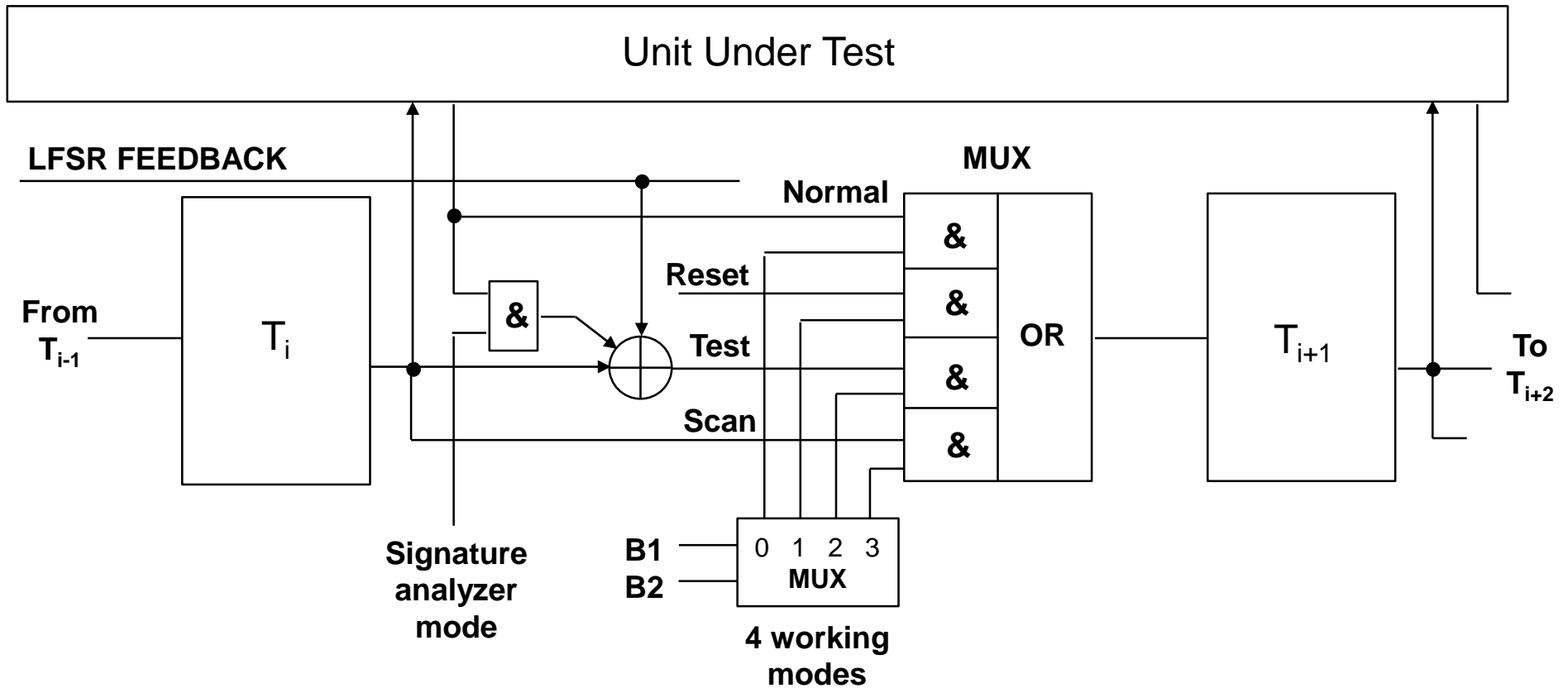

# Pseudorandom Test Generation

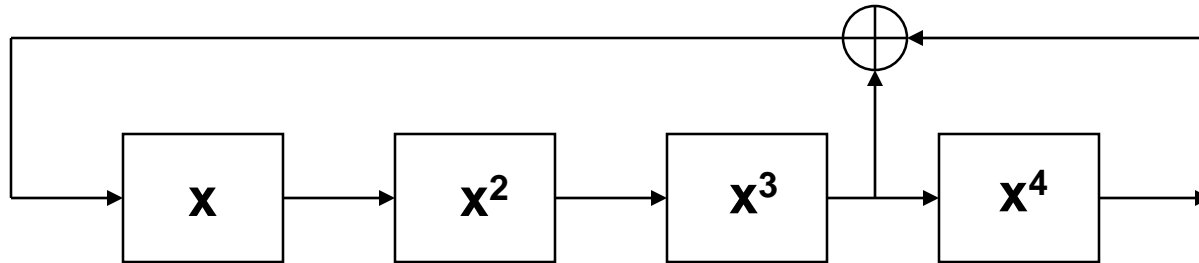

Polynomial:  $P(x) = x^4 + x^3 + 1$

$$\begin{pmatrix} X_4(t+1) \\ X_3(t+1) \\ X_2(t+1) \\ X_1(t+1) \end{pmatrix} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & h_3 & h_2 & h_1 \end{pmatrix} \begin{pmatrix} X_4(t) \\ X_3(t) \\ X_2(t) \\ X_1(t) \end{pmatrix}$$

$\uparrow \quad \uparrow \quad \uparrow$   
 $\vdots \quad \vdots \quad \vdots$   
 $1 \quad 0 \quad 0$

t	x	x <sup>2</sup>	x <sup>3</sup>	x <sup>4</sup>	t	x	x <sup>2</sup>	x <sup>3</sup>	x <sup>4</sup>
1	0	0	0	1	9	0	1	0	1
2	1	0	0	0	10	1	0	1	0
3	0	1	0	0	11	1	1	0	1
4	0	0	1	0	12	1	1	1	0
5	1	0	0	1	13	1	1	1	1
6	1	1	0	0	14	0	1	1	1
7	0	1	1	0	15	0	0	1	1
8	1	0	1	1	16	0	0	0	1

# Theory of LFSR: Primitive Polynomials

---

## Properties of Polynomials:

- **Irreducible polynomial** – cannot be factored, is divisible only by itself
- Irreducible polynomial of degree  $n$  is characterized by:
  - An odd number of terms including 1 term
  - Divisibility into  $1 + x^k$ , where  $k = 2^n - 1$
- Any polynomial with all even exponents can be factored and hence is **reducible**
- An irreducible polynomial of degree  $n$  is **primitive** if it divides the polynomial  $1+x^k$  for  $k = 2^n - 1$ , **but not for any smaller** positive integer  $k$

# Theory of LFSR: Examples

Polynomials of degree  $n=3$  (examples):  $k = 2^n - 1 = 2^3 - 1 = 7$

**Primitive polynomials:**


$$x^3 + x^2 + 1$$

$$x^3 + x + 1$$

The polynomials will divide evenly the polynomial  $x^7 + 1$  but not any one of  $k < 7$ , hence, they are primitive

They are also reciprocal: coefficients are 1011 and 1101

 **Reducible polynomials (non-primitive):**



$$x^3 + 1 = (x + 1)(x^2 + x + 1)$$

$$x^3 + x^2 + x + 1 = (x + 1)(x^2 + 1)$$

**Primitive polynomial**



The polynomials don't divide evenly the polynomial  $x^7 + 1$

# Theory of LFSR: Examples

Is  $x^4 + x^2 + 1$  a primitive polynomial?

Divisibility check:

Irreducible polynomial of degree  $n$  is characterized by:

- An odd number of terms including 1 term?

**Yes, it includes 3 terms**

- Divisibility into  $1 + x^k$ , where  $k = 2^n - 1$

**No, there is remainder**

$x^4 + x^2 + 1$  is non-primitive?

$x^4 + x^2 + 1$	$x^{11} + x^9 + x^5 + x^3$
	$x^{15} + 1$
	$x^{15} + x^{13} + x^{11}$
	<hr style="border: 0.5px solid black;"/>
	$x^{13} + x^{11} + 1$
	$x^{13} + x^{11} + x^9$
	<hr style="border: 0.5px solid black;"/>
	$x^9 + 1$
	$x^9 + x^7 + x^5$
	<hr style="border: 0.5px solid black;"/>
	$x^7 + x^5 + 1$
	$x^7 + x^5 + x^3$
	<hr style="border: 0.5px solid black;"/>
	$x^3 + 1$



# Theory of LFSR: Examples

---

## Comparison of test sequences generated:

### Primitive polynomials

$$x^3 + x + 1$$

$$x^3 + x^2 + 1$$

**100**

**110**

**111**

**011**

**101**

**010**

**001**

**100**

**100**

**010**

**101**

**110**

**111**

**011**

**001**

**100**

### Non-primitive polynomials

$$x^3 + 1$$

$$x^3 + x^2 + x + 1$$

**100**

**010**

**001**

**100**

**010**

**001**

**100**

**010**

**100**

**110**

**011**

**001**

**100**

**110**


**011**

**001**

# Theory of LFSR: Examples

Primitive polynomial


$$x^4 + x + 1$$

 

<b>0001</b>	1011	1001
1000	0101	0100
1100	1010	0010
1110	1101	<b>0001</b>
1111	0110	
0111	0011	

The code **0000** is missing

Zero generation:

 


<b>0000</b>	1011	1001
1000	0101	0100
1100	1010	0010
1110	1101	<b>0001</b>
1111	0110	<b>0000</b>
0111	0011	

 
# Other Problems with Pseudorandom Test

The main motivations of using random patterns are:

- low generation cost
- high initial efficiency



Problem: **low fault coverage**



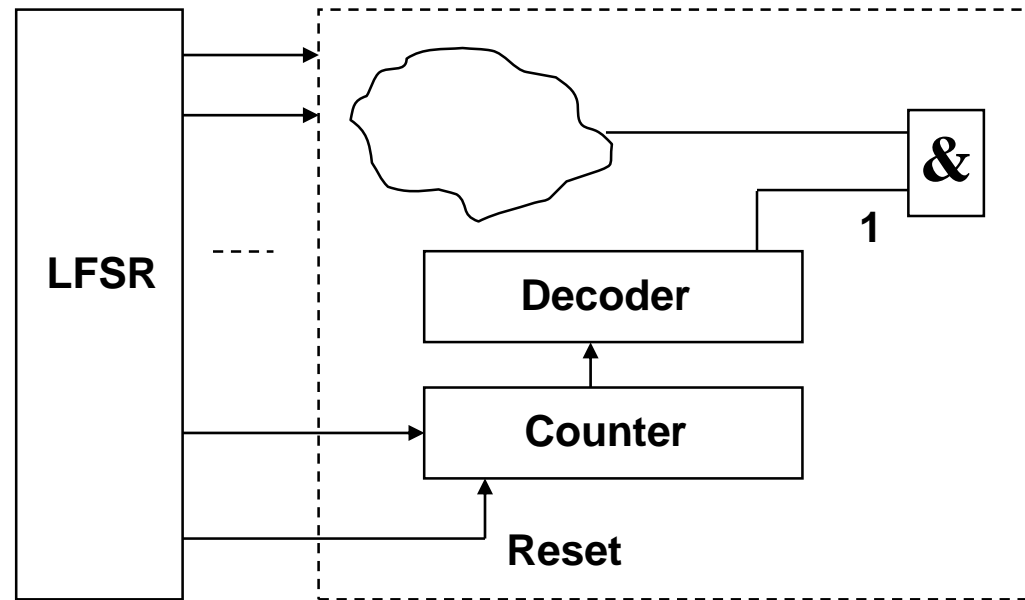


If **Reset = 1** signal has probability 0,5 then counter will not work and 1 for AND gate may never be produced
   
# Sequential BIST

A DFT technique of BIST for sequential circuits is proposed


The approach proposed is based on **all-branches coverage metrics** which is known to be more powerful than all-statement coverage



 
# Problems with BIST: Hard to Test Faults

The main motivations of using random patterns are:


- low generation cost
- high initial efficiency



Problem: **Low fault coverage**

 


**Dream solution:** Find LFSR such that:

 

# BIST: Weighted pseudorandom test

Calculation of signal probabilities:

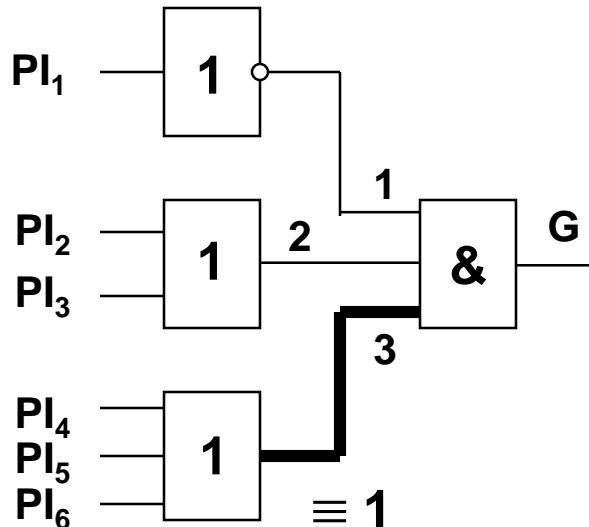

For  $PI_1$  :  $P = 0.15$

For  $PI_2$  and  $PI_3$  :  $P = 0.6$

For  $PI_4 - PI_6$  :  $P = 0.4$

Probability of detecting the fault  $\equiv 1$   
at the input 3 of the gate G:

1) equal probabilities ( $p = 0.5$ ):


$$\begin{aligned} P &= 0.5 * (0.25 + 0.25 + 0.25) * 0.5^3 = \\ &= 0.5 * 0.75 * 0.125 = \\ &= \mathbf{0.046} \end{aligned}$$

2) weighted probabilities:


$$\begin{aligned} P &= 0.85 * \\ &* (0.6 * 0.4 + 0.4 * 0.6 + 0.6^2) * \\ &* 0.6^3 = \\ &= 0.85 * 0.84 * 0.22 = \\ &= \mathbf{0.16} \end{aligned}$$

# BIST: Weighted pseudorandom test
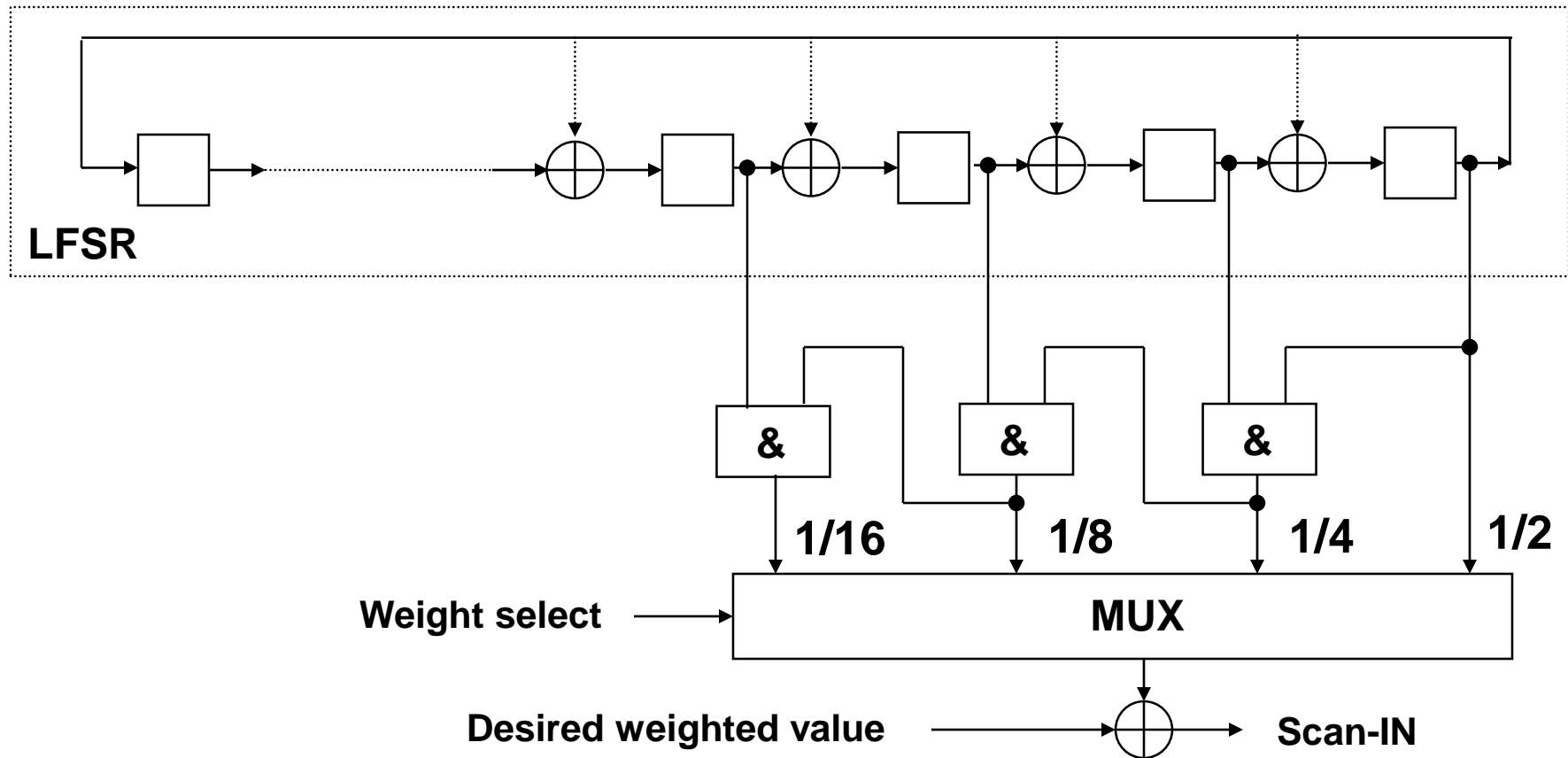
## Hardware implementation of weight generator



# BIST: Signature Analysis

 


The division process can be mechanized using LFSR

The divisor polynomial  $G(x)$  is defined by the feedback connections

Shift creates  $x^5$  which is replaced by  $x^5 = x^3 + x + 1$

IN: 01 010001 → Shifted into LFSR

 


$$\frac{P(x)}{G(x)} = \frac{x^7 + x^3 + x}{x^5 + x^3 + x + 1}$$

**Signature** → 001101 =  $R(x) = x^3 + x^2 + 1$




# BIST: Signature Analysis

## Aliasing:

 


$L$  - test length

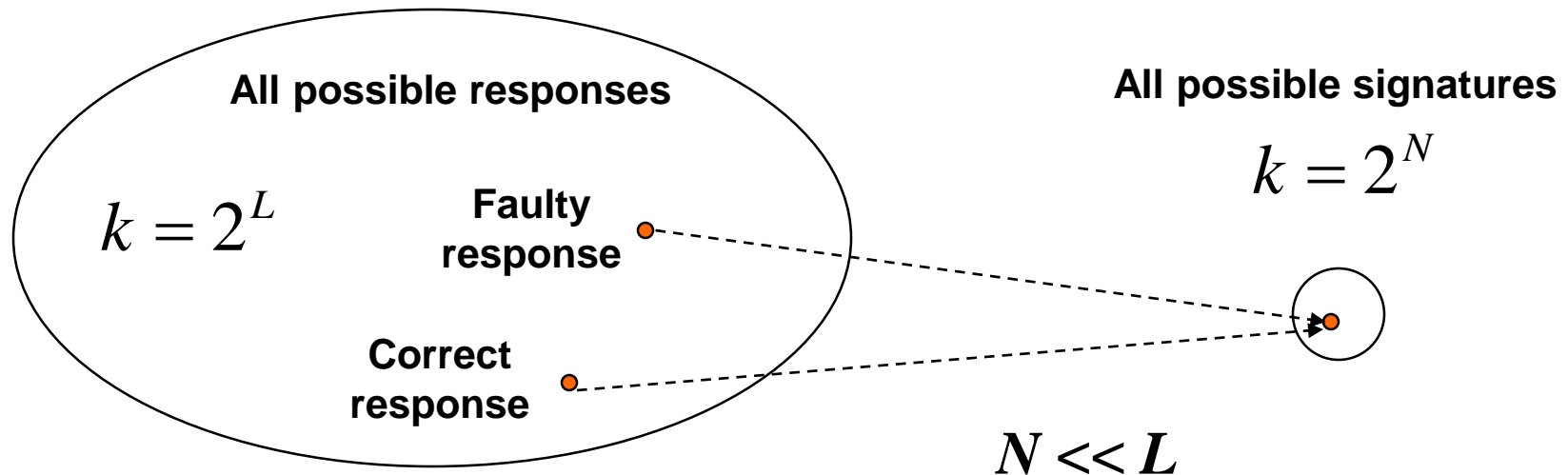$N$  - number of stages in  
Signature Analyzer



# BIST: Signature Analysis

## Aliasing:

 

L - test length

N - number of stages in Signature Analyzer

$k = 2^L$  - number of different possible responses

**No aliasing is possible** for those strings with  $L - N$  leading zeros since they are represented by polynomials of degree  $N - 1$  that are not divisible by characteristic polynomial of LFSR

$2^{L-N} - 1$  - **aliasing is possible**

0000000000000000 ... 00000 **XXXXX**  
L N

**Probability of aliasing:**



$$P = \frac{2^{L-N} - 1}{2^L - 1} \xrightarrow{L \gg 1}$$

$$P = \frac{1}{2^N}$$

# BIST: Signature Analysis

## Parallel Signature Analyzer:



### Single Input Signature Analyser

  


### Multiple Input Signature Analyser (MISR)
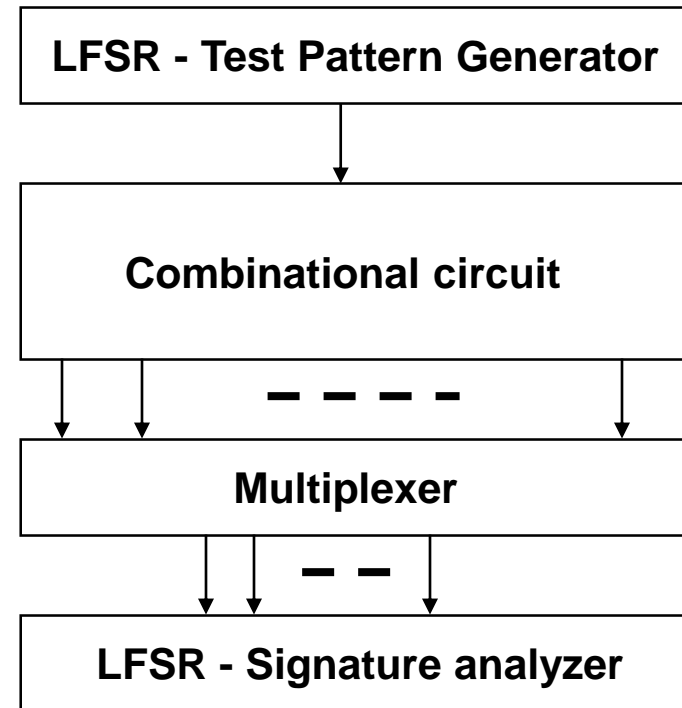 
# BIST: Signature Analysis

Signature calculating for multiple outputs:




# BIST: Joining TPG and SA

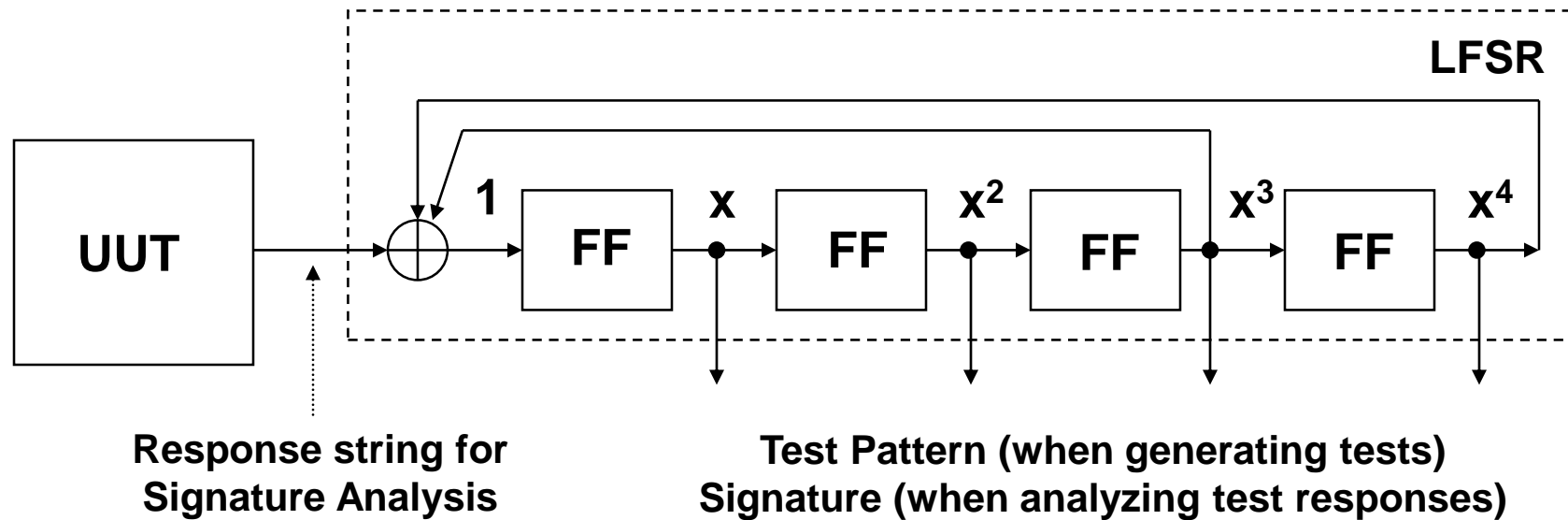

# Hybrid Built-In Self-Test

Deterministic patterns

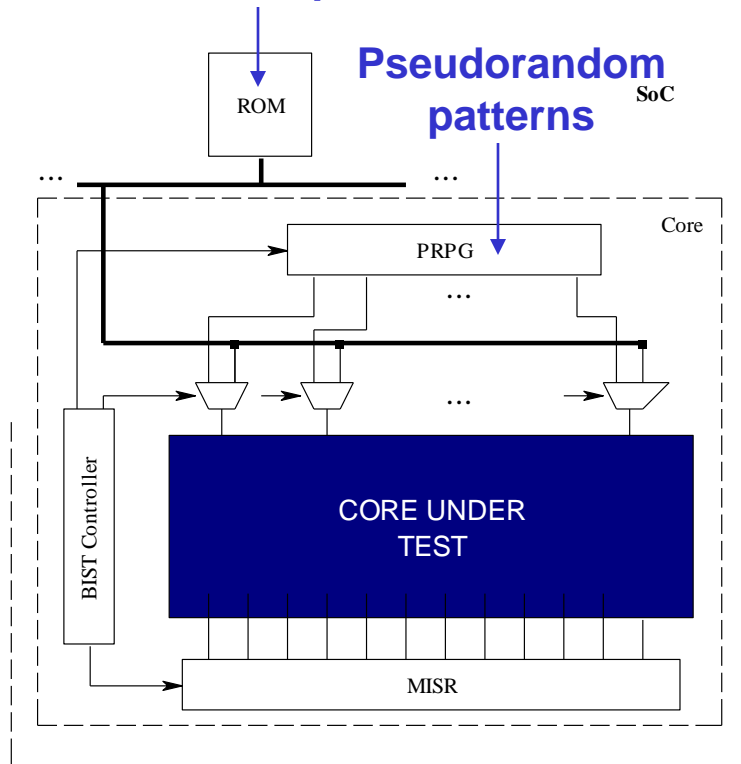

Hybrid test set contains  
**pseudorandom** and  
**deterministic** vectors

Pseudorandom test is improved  
by a stored test set which is  
specially generated to target the  
**random resistant faults**

*Optimization problem:*


Where should be this breakpoint?

Pseudorandom Test

Determ. Test
 
# Optimization of Hybrid BIST

Cost of BIST:  $C_{TOTAL} = \alpha k + \beta t(k)$




<b>PR test length</b>	<b># faults not detected (fast analysis)</b>		<b># tests needed (slow analysis)</b>	
$k$	$r_{DET}(k)$	$r_{NOT}(k)$	$FC(k)$	$t(k)$
1	155	839	15.6%	104
2	76	763	23.2%	104
3	65	698	29.8%	100
4	90	608	38.8%	101
5	44	564	43.3%	99
10	104	421	57.6%	95
20	44	311	68.7%	87
50	51	218	78.1%	74
100	16	145	85.4%	52
200	18	114	88.5%	41
411	31	70	93.0%	26
954	18	28	97.2%	12
1560	8	16	98.4%	7
2153	11	5	99.5%	3
3449	2	3	99.7%	2
4519	2	1	99.9%	1
4520	1	0	100.0%	0


 
# Hybrid BIST with Reseeding

The motivation of using random patterns is:

- low generation cost
- high initial efficiency




  Problem: **low fault coverage** → long PR test






# Store-and-Generate Test Architecture

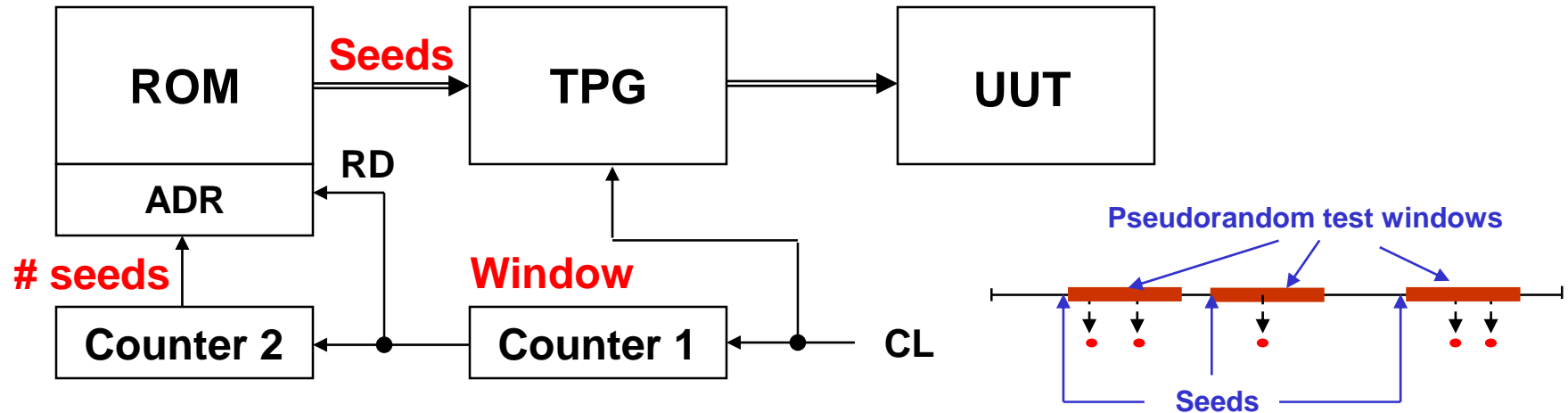


- ROM contains test patterns for hard-to-test faults
- Each pattern  $P_k$  in ROM serves as an initial state of the LFSR for test pattern generation (TPG) - **seeds**
- Counter 1 counts the number of pseudorandom patterns generated starting from  $P_k$  - **width of the windows**
- After finishing the cycle for Counter 2 is incremented for reading the next pattern  $P_{k+1}$  - **beginning of the new window**

# Random BIST vs Functional BIST

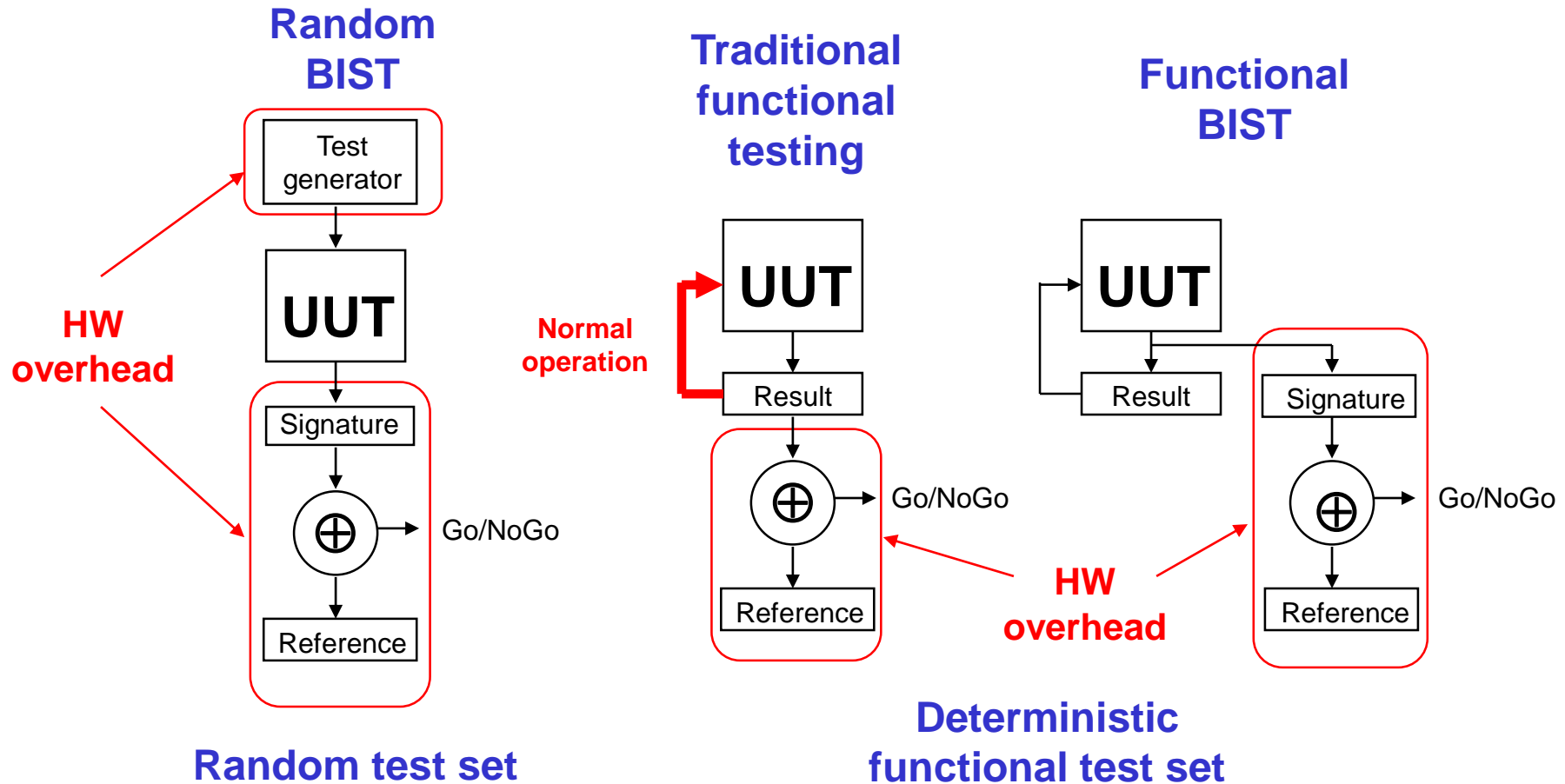


# Example: Functional BIST for Divider

## Functional BIST quality analysis for

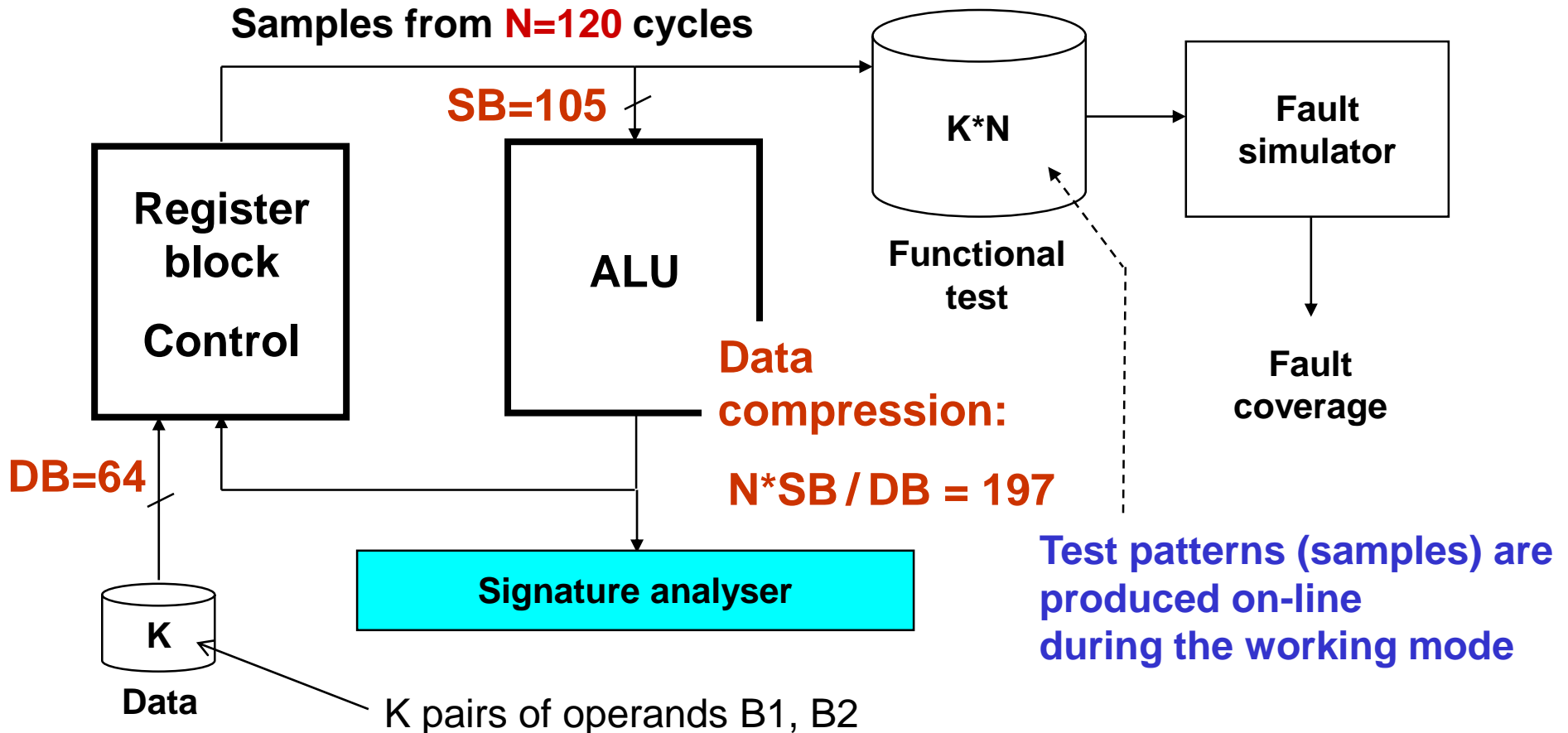


# Hybrid Functional BIST for Divider

## Functional BIST implementation

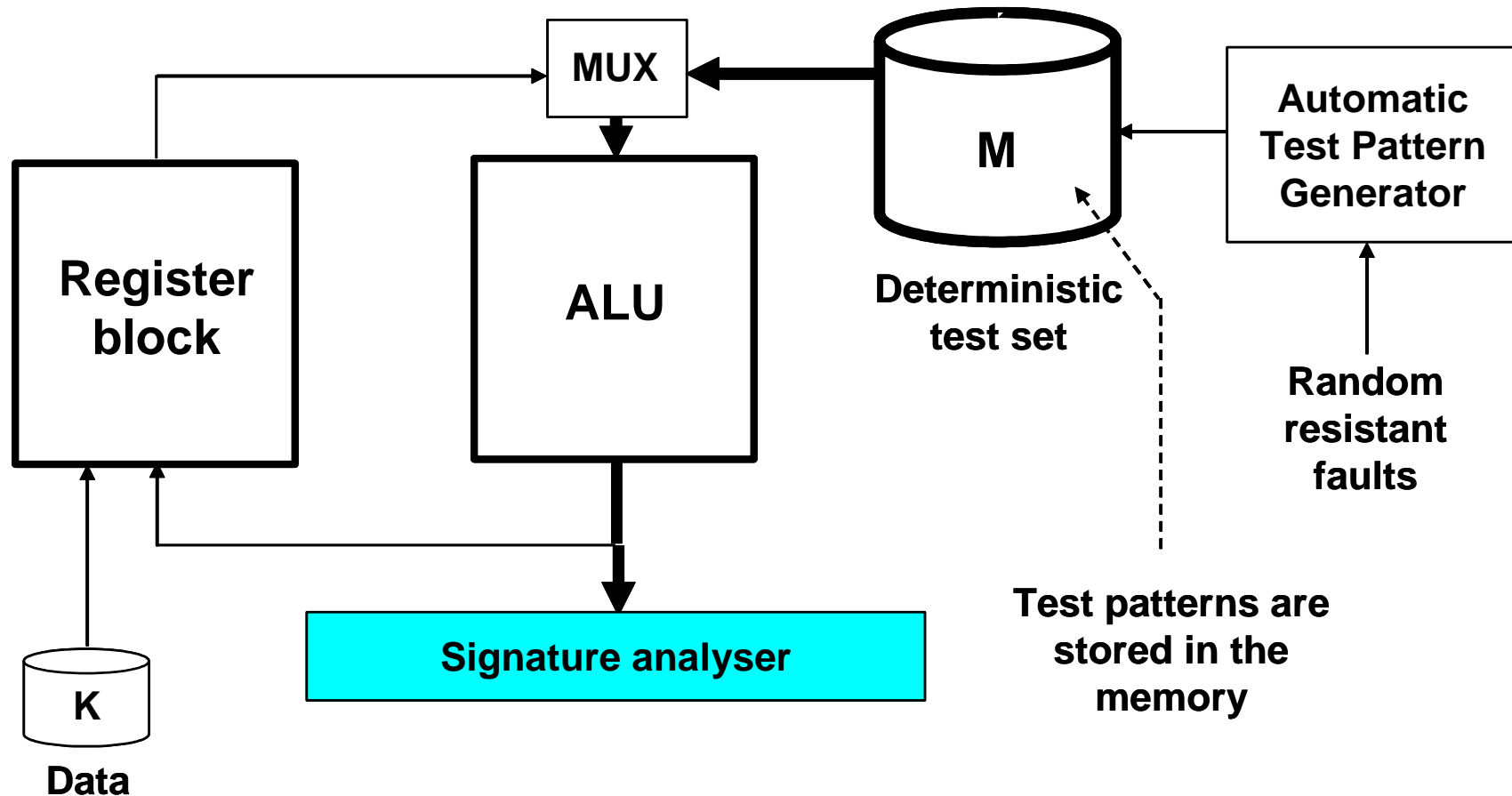


# Functional Self-Test with DFT

## Example: N-bit multiplier

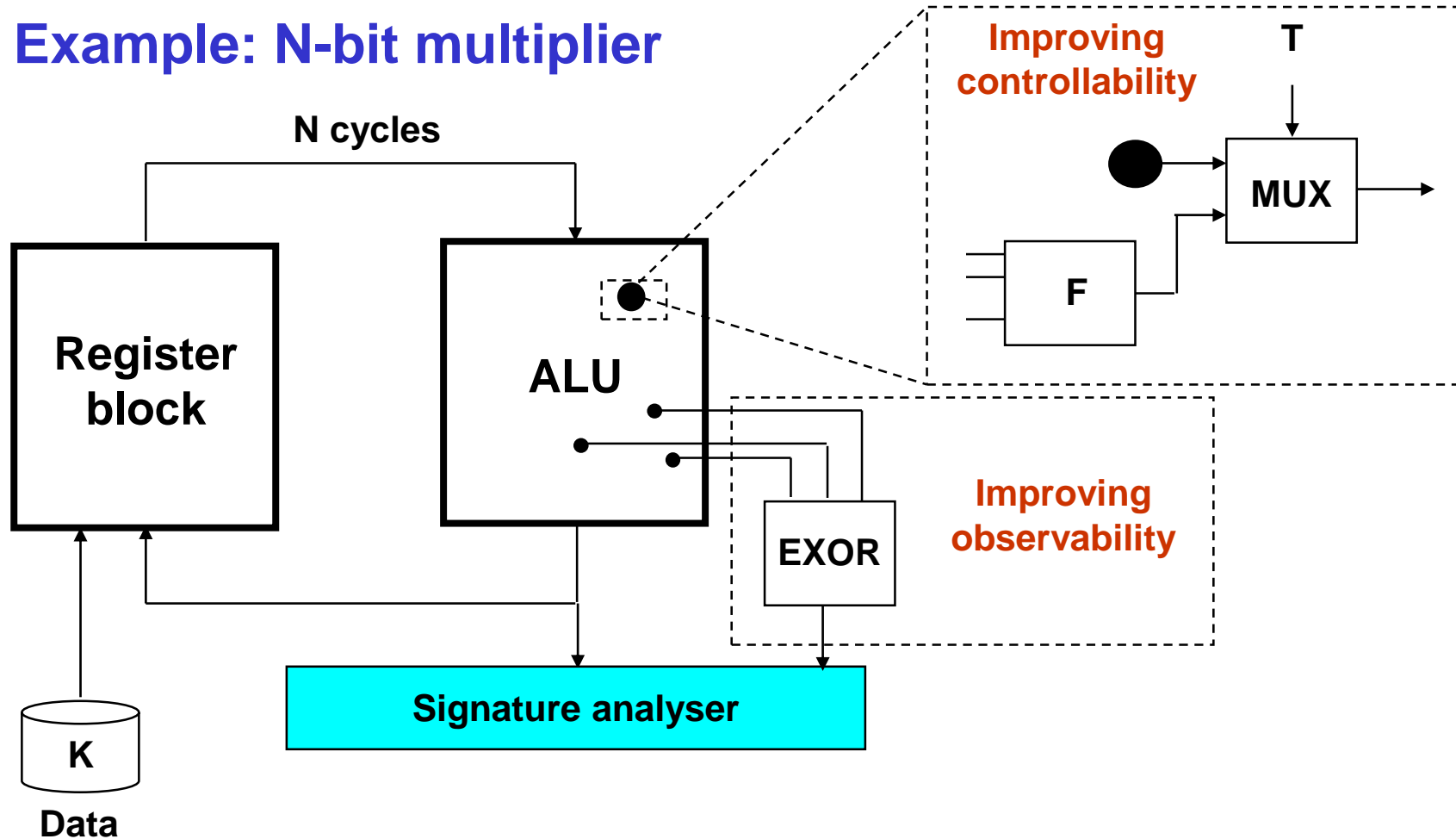


# Embedded BIST Based Fault Diagnosis

## BISD scheme:

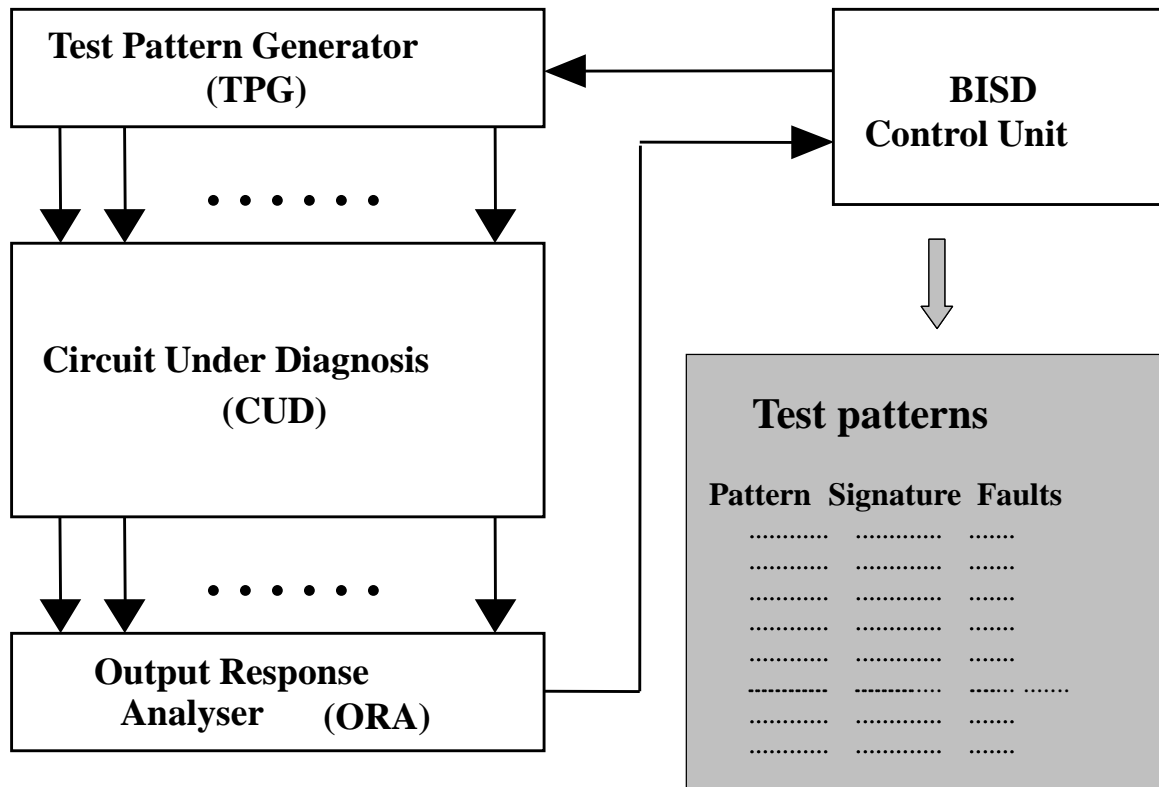


## Pseudorandom test sequence:

 

**Diagnostic Points (DPs)** – patterns that detect new faults  
**Further minimization of DPs** – as a tradeoff with diagnostic resolution

# Built-In Fault Diagnosis

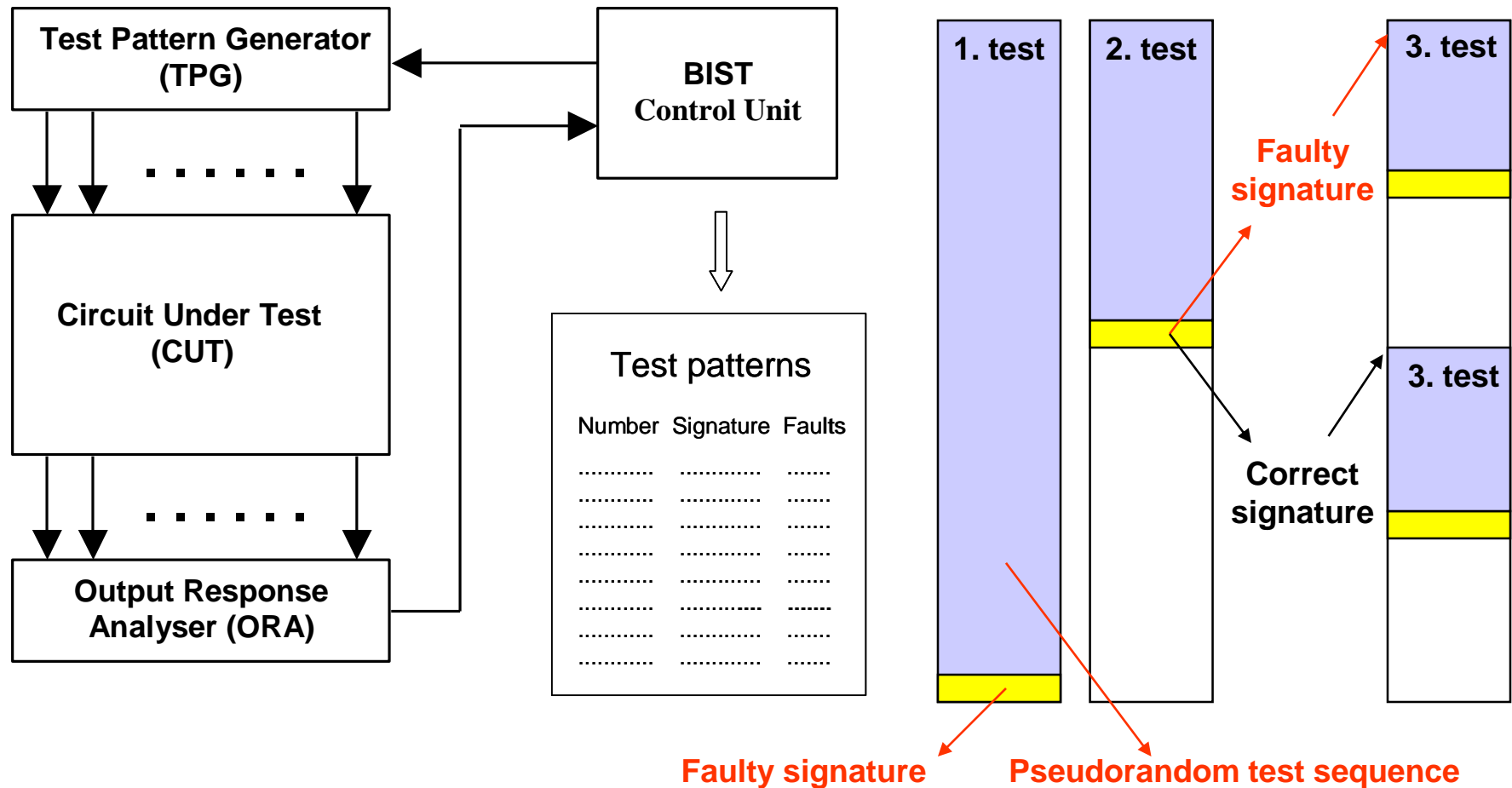

# Built-In Fault Diagnosis


Measuring of information we get from the test:

$$I = -p \log_2 p - (1-p) \log_2 (1-p)$$

Pseudorandom test fault simulation (detected faults)

No	All faults	New faults	Coverage
1	5	5	16.67%
2	15	10	50.00%
3	16	1	53.33%
4	17	1	56.67%
5	20	3	66.67%
6	21	1	70.00%
7	25	4	83.33%
8	26	1	86.67%
9	29	3	96.67%
10	30	1	100.00%

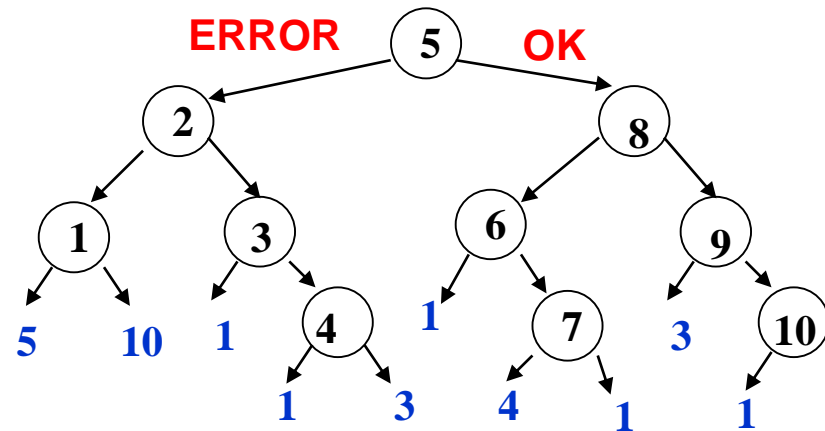Binary search with bisectioning of **test patterns**





Average number of test sessions: 3,3

Average number of clocks: 8,67



 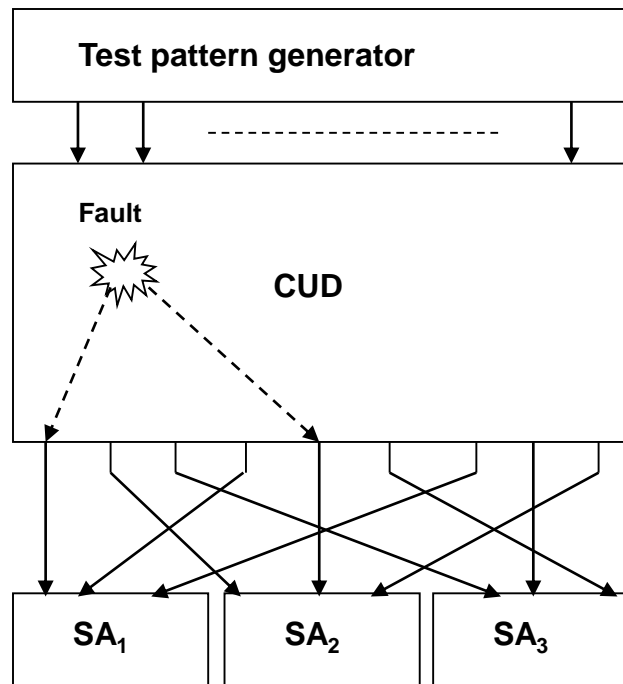
# Built-In Fault Diagnosis

**Diagnosis with multiple signatures**  
(based on reasoning of spacial information):




# Built-In Fault Diagnosis
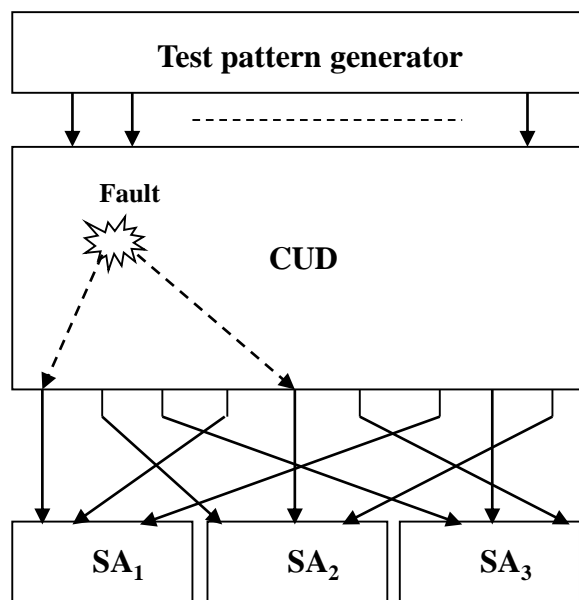
## BIST with multiple signature analyzers



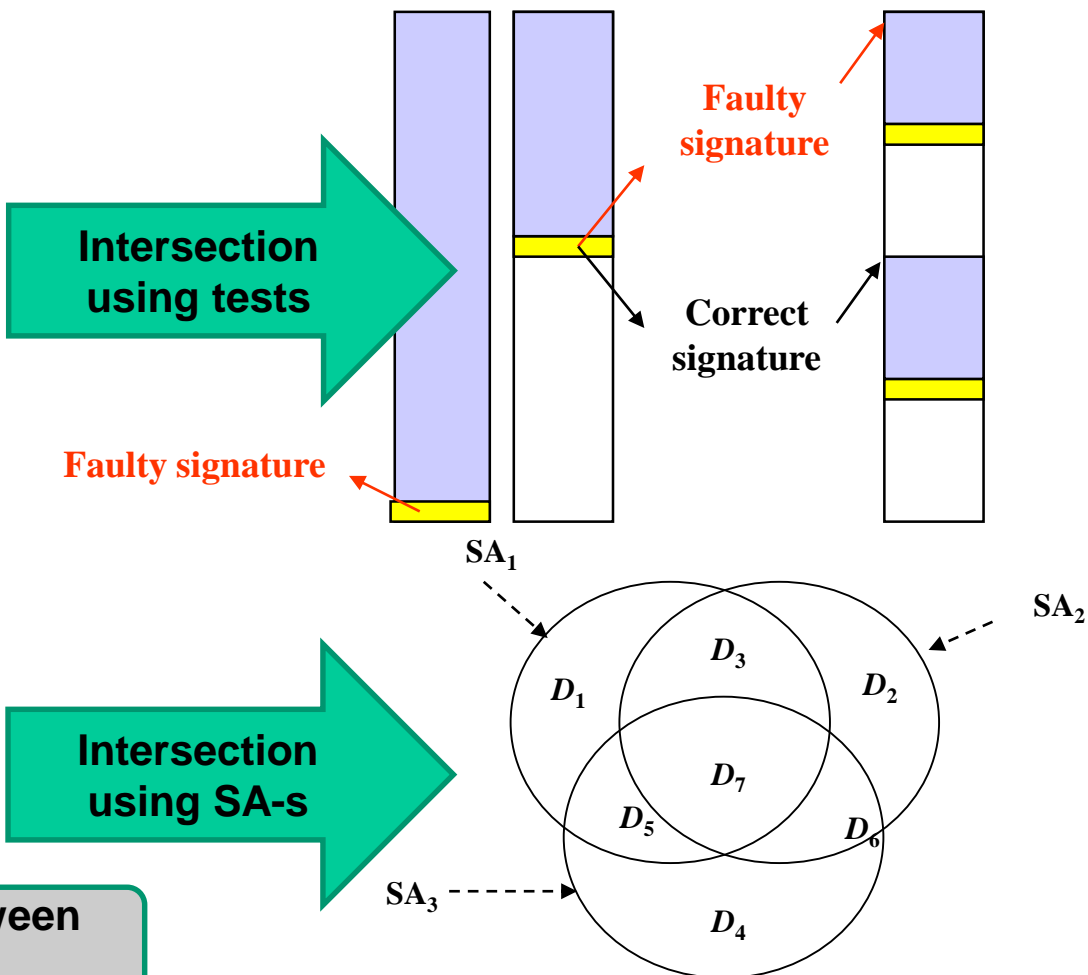Optimization of the interface between CUD and SA-s




# Pseudorandom Testing with LFSR

Primitive polynomial

$$x^4 + x + 1$$

<b>0001</b>	1011	<b>1001</b>
1000	<b>0101</b>	0100
1100	1010	0010
1110	1101	0001
1111	0110	
0111	0011	

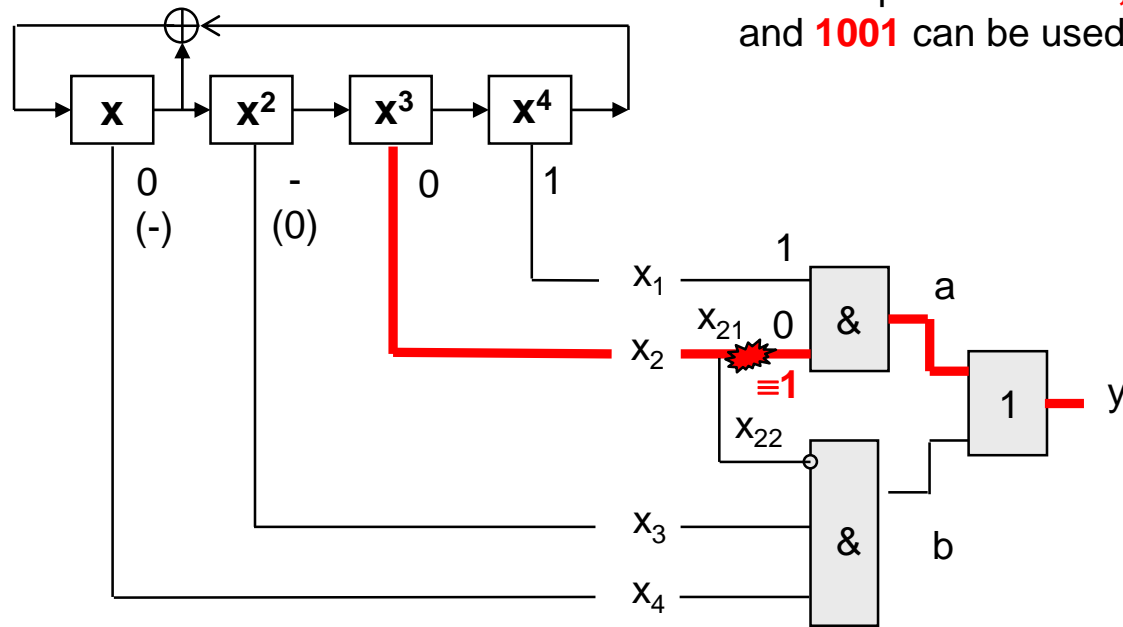


For testing the fault  $x_{21} \equiv 1$   
the test patterns **0001**, **0101**  
and **1001** can be used

# Pseudorandom Testing with LFSR

**Non-primitive polynomial**


$$x^4 + x^2 + 1$$

 


<b>0001</b>	<b>1001</b>	<b>0110</b>
1000	1100	1011
0100	1110	1101
1010	1111	<b>0110</b>
0101	0111	
0010	0011	
<b>0001</b>	<b>1001</b>	



 Be careful: no proper patterns can be generated using the seed 0110




 For testing the fault  $x_{21} \equiv 1$   
the test patterns **0001**, **0101**  
and **1001** can be used



# Deterministic Scan-Path Test


## Test per Clock:

 

- **Initial test set:**

- T1: 1100
- T2: 1010
- T3: 0101
- T4: 1001


- **Test application:**

 

- **Number of clocks = 8 < 20**

# Deterministic Synthesis of LFSR
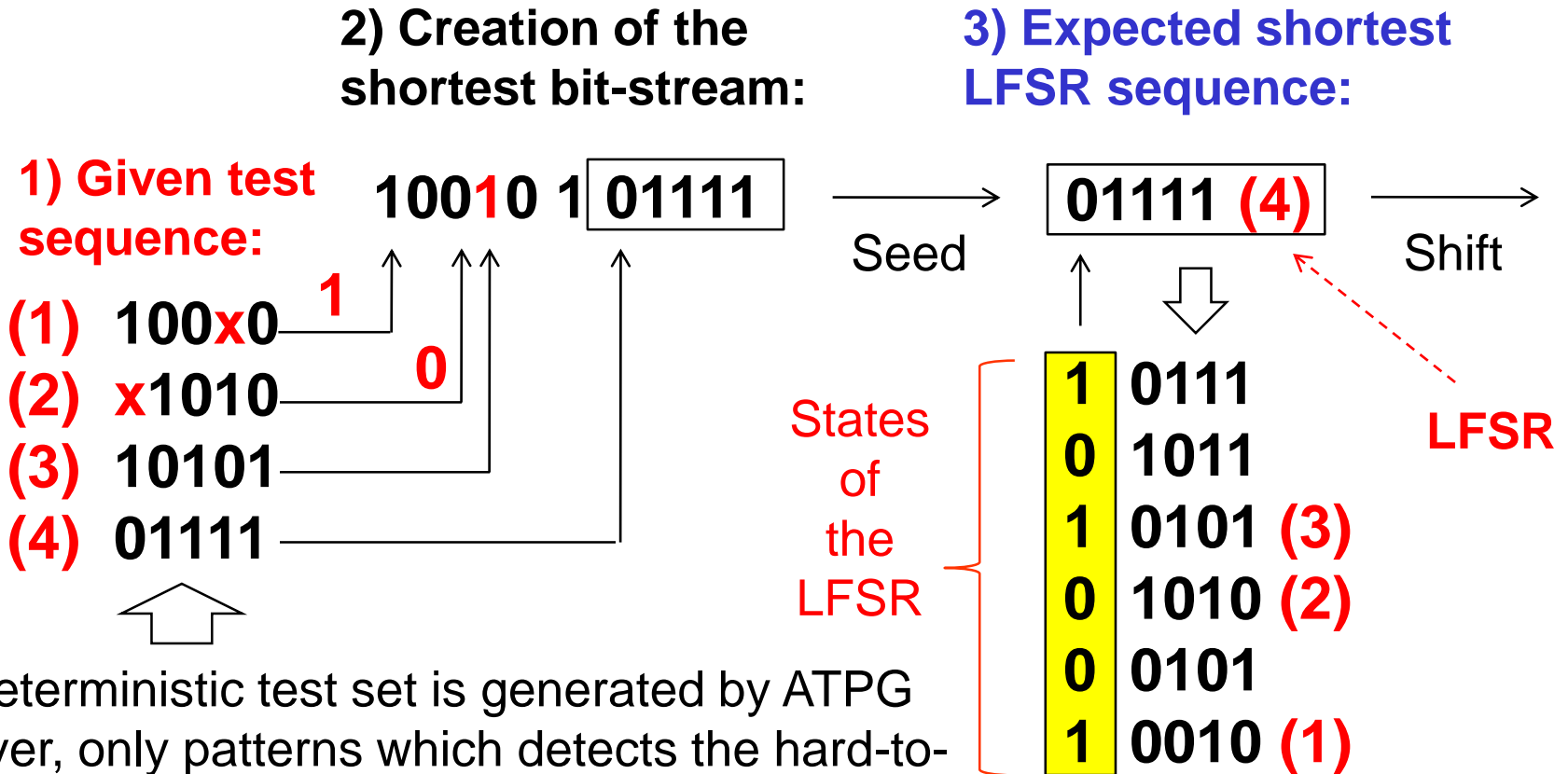
## Generation of the polynomial and seed for the given test sequence



This deterministic test set is generated by ATPG  
 However, only patterns which detects the hard-to-test faults can be chosen

# Deterministic Synthesis of LFSR

Generation of the polynomial and seed for the given test sequence

System of linear equations:  $a_k x_1 \oplus b_k x_2 \oplus c_k x_3 \oplus d_k x_4 \oplus e_k x_5 = f_k$

Expected shortest LFSR sequence:

**01111 (4)**

**1 0111**

**0 1011**

**1 0101 (3)**

**0 1010 (2)**


**0 0101**

**1 0010 (1)**

	$a_k$	$b_k$	$c_k$	$d_k$	$e_k$		$x_j$		$f_k$	
Current state of the LFSR	0	1	1	1	1	$k$	$x_1$	$j$	1	$k$
	1	0	1	1	1	$x$	$x_2$	$=$	0	$k$
	0	1	0	1	1		$x_3$		1	
	1	0	1	0	1		$x_4$		0	
$k=1,2\dots6$	0	1	0	1	0		$x_5$		0	
$j=1,2,,5$	0	1	0	1	0				1	
	0	0	1	0	1				1	

Next input signal into LFSR

We are looking for the values of  $x_i$

 

# Deterministic Synthesis of LFSR

## Generation of the polynomial and seed for the given test sequence

System of linear equations:

$$\begin{array}{l}
 1 \\
 2 \\
 3 \\
 4 \\
 5 \\
 6
 \end{array}
 \left| \begin{array}{l}
 \mathbf{01111} \\
 \mathbf{10111} \\
 \mathbf{01011} \\
 \mathbf{10101} \\
 \mathbf{01010} \\
 \mathbf{00101}
 \end{array} \right|
 \times
 \left| \begin{array}{l}
 \mathbf{x}_1 \\
 \mathbf{x}_2 \\
 \mathbf{x}_3 \\
 \mathbf{x}_4 \\
 \mathbf{x}_5
 \end{array} \right|
 =
 \left| \begin{array}{l}
 \mathbf{1} \\
 \mathbf{0} \\
 \mathbf{1} \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{1}
 \end{array} \right|$$

Solving the equation by Gaussian elimination with swapping of rows

Rows:

1,2,4,6  
4,6  
1,3  
2,4  
1,3,6

Results:

$$\begin{array}{l}
 \mathbf{01000} \\
 \mathbf{10000} \\
 \mathbf{00100} \\
 \mathbf{00010} \\
 \mathbf{00001} \\
 \mathbf{00001}
 \end{array}
 \left| \begin{array}{l}
 \mathbf{x}_1 \\
 \mathbf{x}_2 \\
 \mathbf{x}_3 \\
 \mathbf{x}_4 \\
 \mathbf{x}_5
 \end{array} \right|
 =
 \left| \begin{array}{l}
 \mathbf{0} \\
 \mathbf{1} \\
 \mathbf{0} \\
 \mathbf{0} \\
 \mathbf{1} \\
 \mathbf{1}
 \end{array} \right|
 \begin{array}{l}
 \mathbf{f}_k \\
 \mathbf{f}_2 \\
 \mathbf{f}_3
 \end{array}$$

$$a_k x_1 \oplus b_k x_2 \oplus c_k x_3 \oplus d_k x_4 \oplus e_k x_5 = f_k, k = 1, 2, \dots, 6$$

$$\begin{array}{ll}
 \mathbf{k=2} \ (4) \ 10101 \ 0 & \mathbf{k=3} \ (1) \ 01111 \ 1 \\
 \quad \quad \quad (6) \ 00101 \ 1 & \quad \quad \quad (3) \ 01011 \ 1 \\
 (4 \oplus 6) \ \mathbf{10000} \ \mathbf{1} & (1 \oplus 3) \ \mathbf{00100} \ \mathbf{0}
 \end{array}$$

4) Solution:  $x_1 \ x_2 \ x_3 \ x_4 \ x_5$   
1 0 0 0 1



# Deterministic Synthesis of LFSR


Embedding deterministic test patterns into LFSR sequence:

4) Solution:  $x_1 x_2 x_3 x_4 x_5$   
 1 0 0 0 1



5) Polynomial:  $x^5 + x + 1$  Seed: 01111

LFSR sequence:

 

Given  
deterministic  
test  
sequence:

(1) 100x0  
 (2) x1010  
 (3) 10101  
 (4) 01111

(1) 01111 (4)

(2) 10111

(3) 01011

(4) 10101 (3)

(5) 01010 (2)

(6) 00101

(7) 10010 (1)

# Exam Tasks - 1

---

## Testability measures: probability calculation

1. Calculation of the **probability of a signal** (7,8)
2. Comparison of probability calculation with **Parker McCluskey and linear methods** (7,8)
3. Calculation of the **probabilistic testability of a fault** (7,9)
4. Calculation of the **length of pseudorandom test** for detecting a fault (7,9)
5. Calculating of signal probabilities with **Cutting Method** (10,11)
6. Calculating of signal probabilities with the method of **Conditional Probabilities** (12,13)

# Exam Tasks - 2

---

## Design for testability:

1. Comparison of test lengths for detecting a fault with and without of DFT ([test point insertion](#)) (7,9,14,25)
2. Calculation of test lengths (number of LFSR clocks) for different ad hoc designs: [multiplexing](#) of observers, [de-multiplexing](#) of control, [time sharing](#) (15-20)
3. Comparison of test lengths (number of LFSR clocks) for [ad hoc and scan-based DFT](#) solutions (15-20, 28)

# Exam Tasks - 3

---

## Built-in Self-Test:

1. Calculation of the test sequence for a given **LFSR polynomials** (45,49)
2. Design of **LFSR reconfiguration** logic for given functions (43,44)
3. Determination if the LFSR polynomial is **primitive** or not (46,47,48)
4. Design a LFSR for a **weighted pseudorandom testing** with given probabilities (54,55)
5. Synthesis of an LFSR which is able to cover a given test pattern set (77-81)
6. Synthesis of an LFSR which is able to detect a given set of faults; generate the test sequence (75, 76)